

Register Transfer Level

CSE3201

RTL

- A digital system is represented at the register transfer level by these three components
 1. The set of registers in the system
 2. The operation that are performed on the data stored in the registers
 3. The control that supervises the sequence of operations in the system.
- The operations executed on the information stored in the registers are elementary operations and performed in parallel during one clock cycle.

RTL

- Comma is used to separate 2 or more operations that are executed in the same time

If (T3=1) then ($R2 \leftarrow R1$, $R1 \leftarrow R2$)

- That is possible with registers that have edge triggered flip-flop
- Increment R1 then store it in R2

$R2 \leftarrow R1 + 1$

RTL in HDL

```
assign S=A+B;
```

```
always @(A or B)  
    S=A+B;
```

Continuous assignment,
for combinational
circuits only, output can
not be a reg

```
always @ (posedge clock)  
    begin  
        RA=RA+RB;  
        RD=RA;  
    end
```

Blocking procedural
assignment, new value of
RA is assigned to RD

```
always @ (negedge clock)  
    begin  
        RA<=RA+RB;  
        RD<=RA;  
    end
```

Non-blocking procedural
assignment, old value of
RA is assigned to RD

HDL Operations

- Arithmetic: + - * / %
- Logic (bit wise): ~ & | ^
- Logical ! && ||
- Shift >> << { , }
- Relational > < == != >= <=
- In shifting, the vacant bits are filled with zeros
- L

Loop Statements

- | | |
|-----------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------------------|
| <pre>integer count initial begin count = 0; while (count < 16) #5 count = count+1; end</pre> | <pre>initial begin clock = 1'b0; end repeat (16) #5 clock = ~ clock; end</pre> |
|-----------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------------------|

Loop Statements


```
module decoder
    input [1:0] IN;
    output [3:0] Y;
    reg [3:0] Y;
    integer I;
    always @(IN)
        for (I=0; I<=3; I=I+1)
            if (IN == I) Y[I]=1;
            else Y[I]=0;
endmodule
```

Synthesis

- Logic synthesis tools interpret the source code and translate it into an optimized gate structure.
- Statement like assign **s=a&b** is translated into an AND gate
- Statement like assign **s=a+b** is translated into adder
- Statement like assign **y=s? in_1:in_2** is translated into a 2-to-1 multiplexer

Synthesis

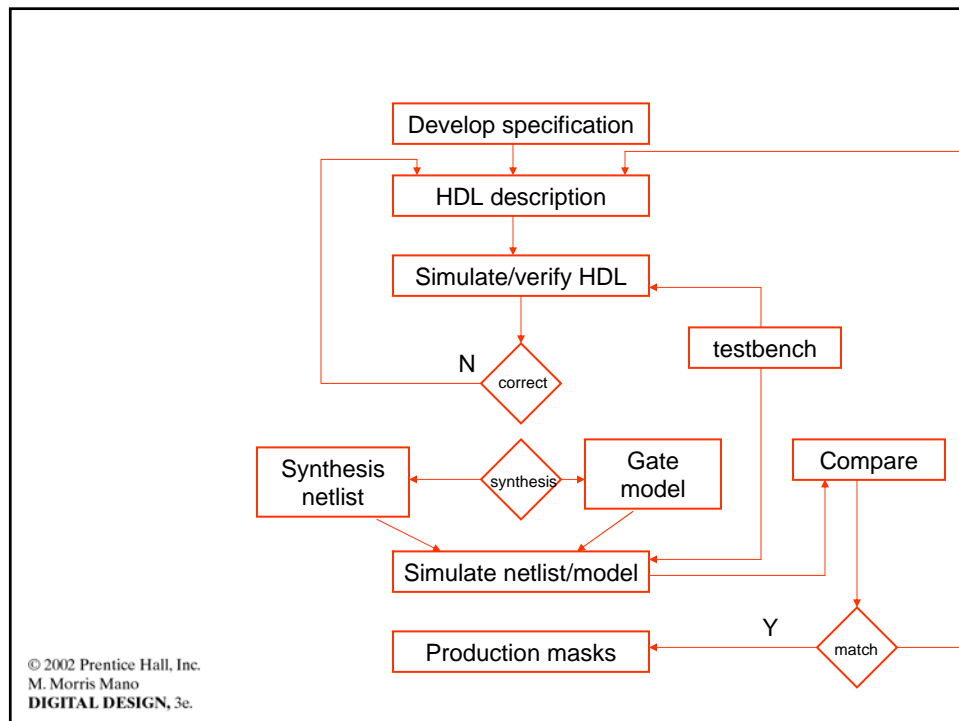- Always may imply combinational or sequential circuit based on the event control expression (level or edge)
always @(L1 or L0 or S)
 if (S) Y=l1;
 else Y=l0;
Is translated into a 2-to-1 multiplexer
- If the event control is “posedge”, that is a synchronous sequential circuit



Algorithmic State Machine (ASM)

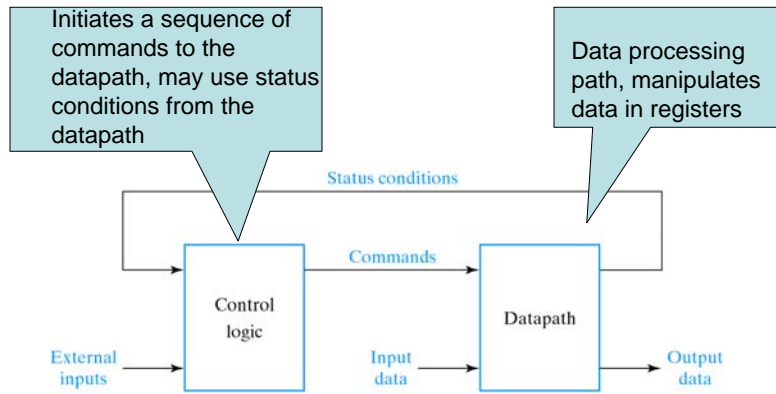


Fig. 8-2 Control and Datapath Interaction

© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

ASM

- ASM is similar to flowchart in the sense that it specifies a sequence of procedural steps and decision paths for an algorithm.
- However, ASM is interpreted differently than a flowchart. While the flow chart is interpreted as a sequence of operations, ASM describes the sequence of events as well as the timing relationship between the states (as we will see shortly).

State Box

 


Fig. 8-3 State Box

The state is given a symbolic name (T_3) (name may be inside the box)

Binary code for the assigned state (011)

The operations that are performed in this state $R \leftarrow 0$; and START could be an output signal is generated to start some operation

Operation happens when the machine makes a transition from T_3 to next state

Decision Box

 


Fig. 8-4 Decision Box

Conditional Box

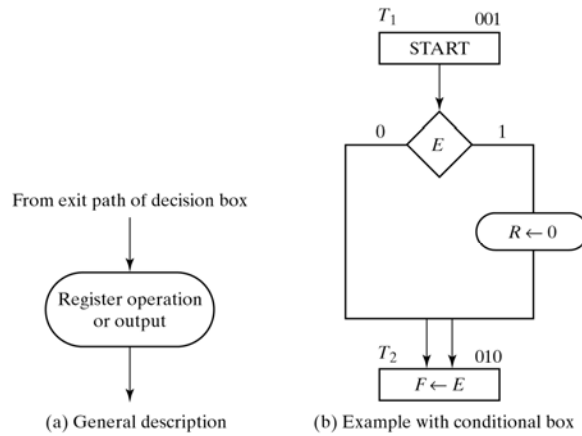


Fig. 8-5 Conditional Box


Input to the decision box must come from one of the exit paths of a decision box.

The register operation or outputs listed inside the conditional box are generated during a given state, if the input condition is satisfied of course

Depending on E, R is cleared or left unchanged

One entrance

ASM Block

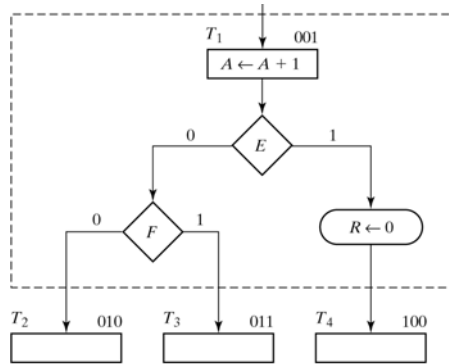

If flow chart, A is incremented, then E is tested

 


Fig. 8-7 State Diagram Equivalent to the ASM Chart of Fig. 8-6

ASM block is a structure consisting of one state box and all the decision and conditional boxes connected to its exit path.

Each block in the ASM describes the state of the system during one clock-pulse interval.

The operations within the state and conditional boxes are executed while the system is in state T_1 . The same clock pulse transfer the system into T_2 , T_3 , or T_4 .

Timing Consideration


 


Fig. 8-8 Transition Between States


Design Example

- Design a system with 2 flip-flops E and F, and one 4 bit binary counter (A_3, A_2, A_1, A_0).
- A start signal initiates the operation by clearing A and F.
- Then the counter is incremented by one starting from the next clock pulse and continues to increment until the operation stops. A_3 and A_4 determine the operations.
 - If $A_2 = 0$, E is cleared and continue
 - If $A_2 = 1$, E is set; then if $A_3 = 0$ continue, if $A_3 = 1$ F is set to 1 on the next clock cycle.
- If $start = 0$, the system stays in the initial state, otherwise repeat


Example

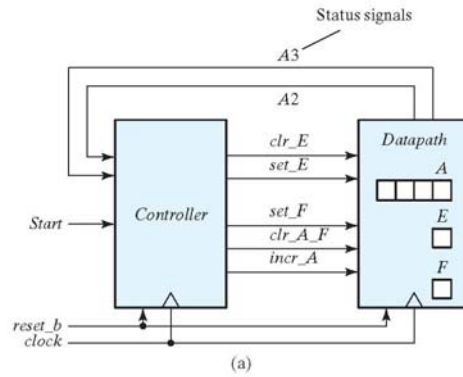

 Note: A3 denotes A[3],
A2 denotes A[2],
<= denotes nonblocking assignment
reset_b denotes active-low reset condition



Asynchronous reset

 

Synchronous reset

 



Table 8.3
Sequence of Operations for Design Example

Counter				Flip-Flops		Conditions	State
A_3	A_2	A_1	A_0	E	F		
0	0	0	0	1	0	$A_2 = 0, A_3 = 0$	S_1
0	0	0	1	0	0		
0	0	1	0	0	0		
0	0	1	1	0	0		
0	1	0	0	0	0	$A_2 = 1, A_3 = 0$	
0	1	0	1	1	0		
0	1	1	0	1	0		
0	1	1	1	1	0		
1	0	0	0	1	0	$A_2 = 0, A_3 = 1$	
1	0	0	1	0	0		
1	0	1	0	0	0		
1	0	1	1	0	0		
1	1	0	0	0	0	$A_2 = 1, A_3 = 1$	S_2
1	1	0	1	1	0		
1	1	0	1	1	1		S_idle


Figure Number: Table 08.03
Macro/Cells:
Digital Design, 4e



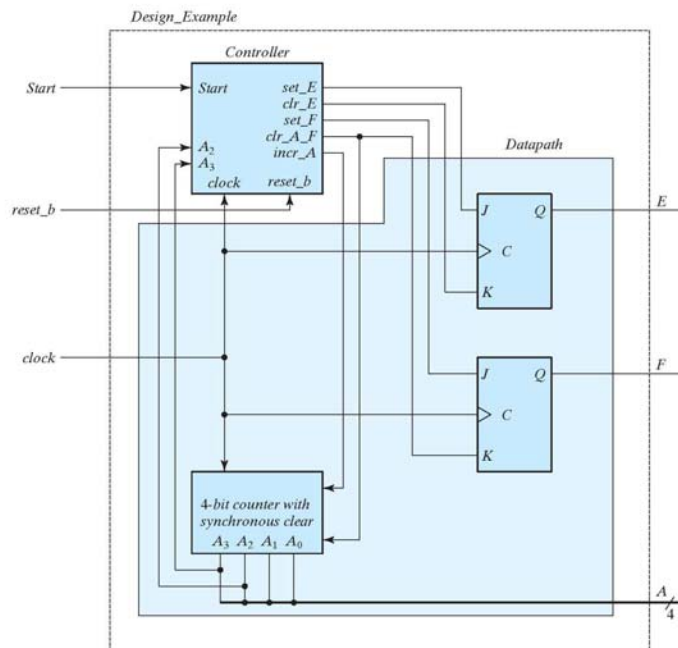©2007 by Prentice Hall, Inc.
A Pearson Company



RTL Description

 

$S_idle \rightarrow S_1, clr_A_F:$ $A \leftarrow 0, F \leftarrow 0$
 $S_1 \rightarrow S_1, incr_A:$ $A \leftarrow A + 1$
 if ($A_2 = 1$) then set_E: $E \leftarrow 1$
 if ($A_2 = 0$) then clr_E: $E \leftarrow 0$
 $S_2 \rightarrow S_idle, set_F:$ $F \leftarrow 1$

(b)

Table 8.4
State Table for the Controller of Fig. 8.10

Present-State Symbol	Present State		Inputs			Next State		Outputs				
	G ₁	G ₀	Start	A ₂	A ₃	G ₁	G ₀	set_E	clr_E	set_F	clr_A_F	incr_A
S_idle	0	0	0	X	X	0	0	0	0	0	0	0
S_idle	0	0	1	X	X	0	1	0	0	0	1	0
S_1	0	1	X	0	X	0	1	0	1	0	0	1
S_1	0	1	X	1	0	0	1	1	0	0	0	1
S_1	0	1	X	1	1	1	1	1	0	0	0	1
S_2	1	1	X	X	X	0	0	0	0	1	0	0

$$DG_1 = S_1 A_2 A_3$$

$$DG_0 = S_1 + S_idle \text{ Start}$$


$$\text{Set_E} = S_1 A_2$$

$$\text{Clr_E} = S_1 A'_2$$

$$\text{Set_F} = S_2$$

$$\text{Clr_A_F} = \text{Start } S_idle$$

$$\text{Incr_A} = s_1$$

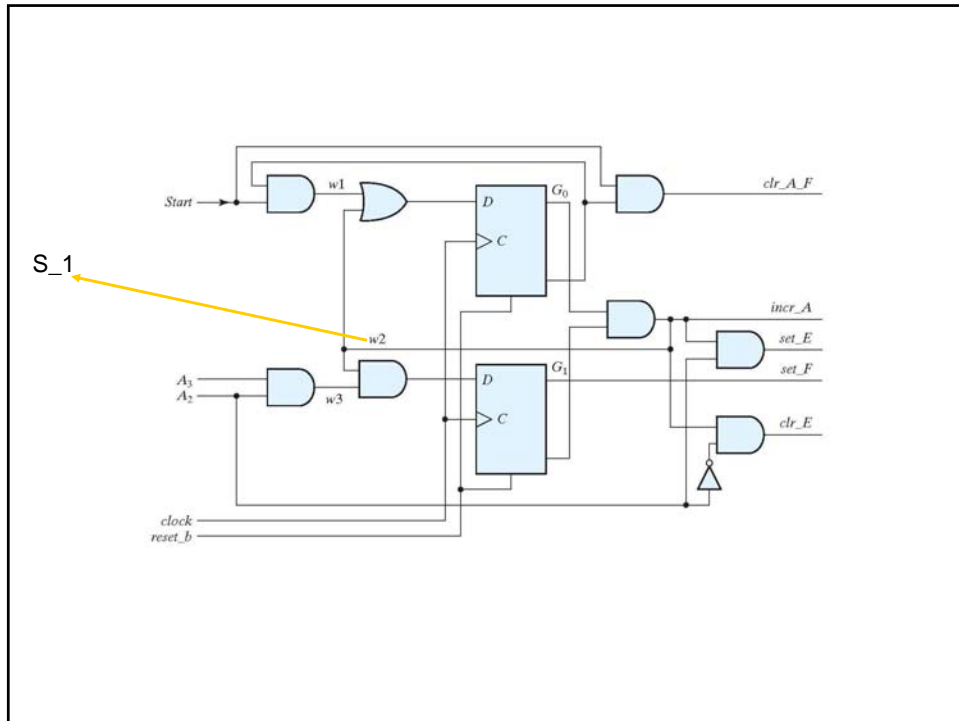

HDL Description

- The description could be on three different levels
 - Behavioral description on the RTL level
 - Behavior description on the algorithmic level
 - Structural description
- Note that the algorithmic level, is used only to verify the design *ideas* in the early stages. Some of the constructs might not be *synthesizable*
- Following RTL behavior description


Binary Multiplier

- We did this before using combinational circuit (adders, gaters, ..).
- Use one adder and shift registers.
- Instead of shifting multiplicand to the left, shift the partial product to the right.


23	10111
19	10011

	10111
	10111
	00000
	00000
	10111



437	110110101

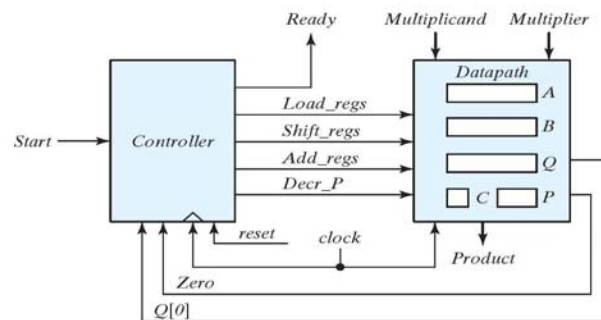

(a)

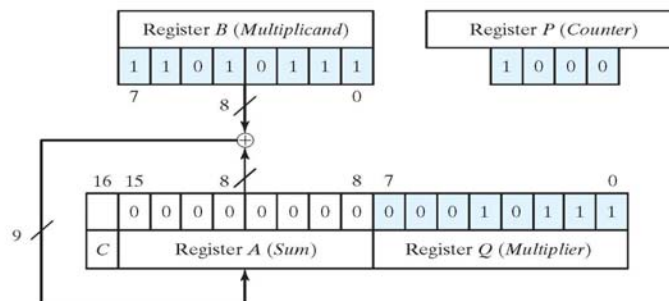

(b)

 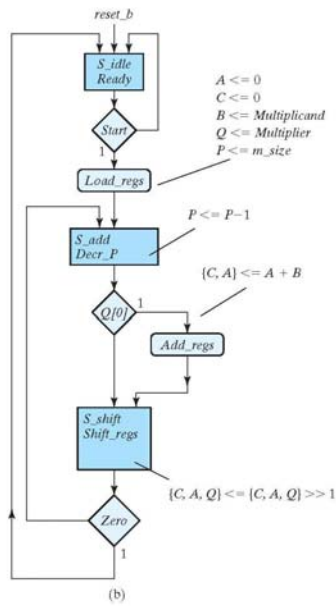

State Transition		Register Operations
<u>From</u>	<u>To</u>	
S_idle		Initial state
S_idle	S_add	$A \leq 0, C \leq 0, P \leq dp_width$
S_add	S_shift	$P \leq P - 1$ if $(Q[0])$ then $(A \leq A + B, C \leq C_{out})$
S_shift		shift right $\{CAQ\}$, $C \leq 0$


(b)

Table 8.6
State Assignment for Control


State	Binary	Gray Code	One-Hot
<i>S_idle</i>	00	00	001
<i>S_add</i>	01	01	010
<i>S_shift</i>	10	11	100

Table 8.7
State Table for Control Circuit

Present-State Symbol	Present State		Inputs			Next State		<i>Ready</i>	<i>Load_regs</i>	<i>Decr_P</i>	<i>Add_regs</i>	<i>Shift_regs</i>
	<i>G</i> ₁	<i>G</i> ₀	<i>Start</i>	<i>Q</i> [0]	<i>Zero</i>	<i>G</i> ₁	<i>G</i> ₀					
<i>S_idle</i>	0	0	0	X	X	0	0	1	0	0	0	0
<i>S_idle</i>	0	0	1	X	X	0	1	1	1	0	0	0
<i>S_add</i>	0	1	X	0	X	1	0	0	0	1	0	0
<i>S_add</i>	0	1	X	1	X	1	0	0	0	1	1	0
<i>S_shift</i>	1	0	X	X	0	0	1	0	0	0	0	1
<i>S_shift</i>	1	0	X	X	1	0	0	0	0	0	0	1

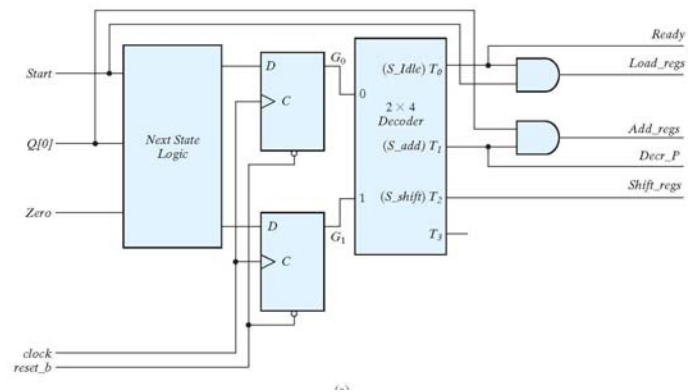


Using Sequence register and a decoder

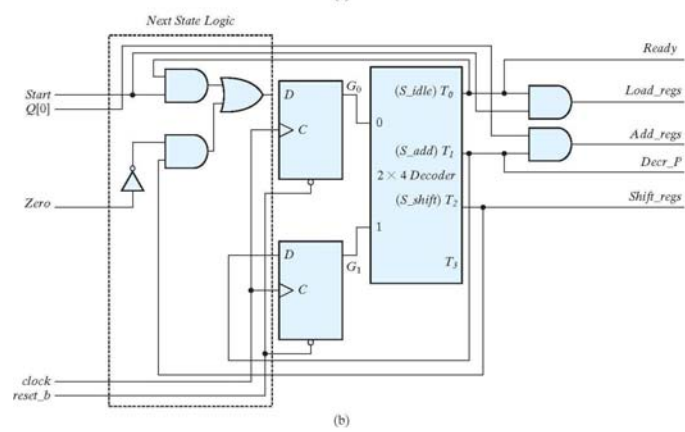

One-Hot Design

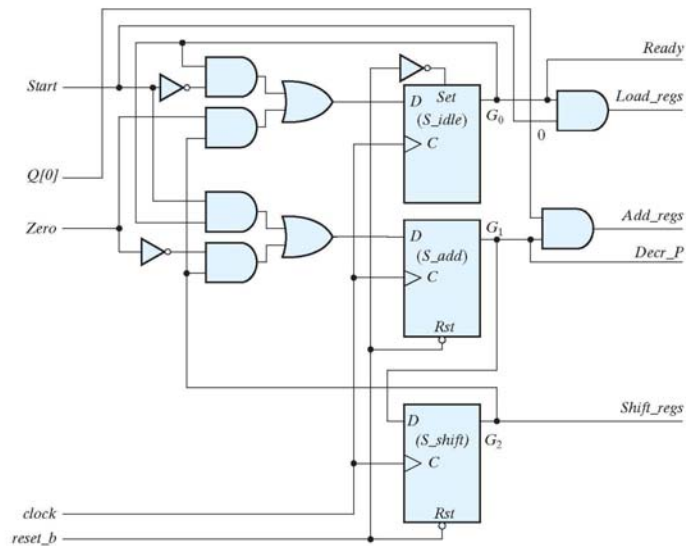- Every state is represented by a flip flop
- Only one contains a value of 1 at any time
- Simple but uses more FF



Design with multiplexers

- The previous design consists of flip-flops, decoder, and gates.
- Replacing gates with multiplexers results in a regular pattern of the design.
 - First level contains multiplexers (possibly added gates, but only one level).
 - The second level is the registers to hold the present state information
 - The last stage has a decoder that provides a separate output for every state

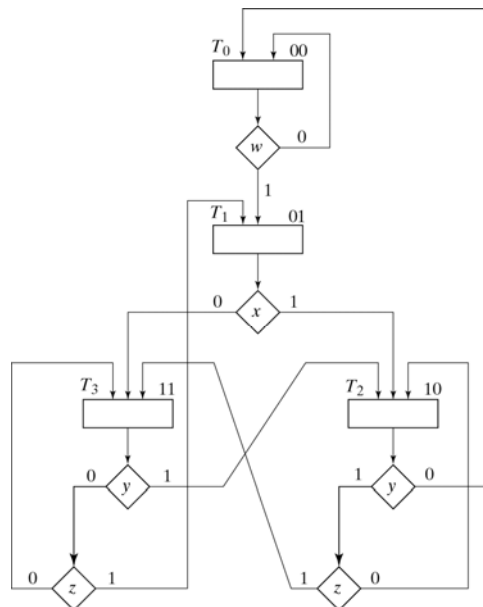


Fig. 8-19 Example of ASM Chart with Four Control Inputs

Multiplexer input condition

Present State		next State		I/P	inputs	
G1	G0	G1	G0	cond.	MUX1	MUX2
0	0	0	0	w'		
0	0	0	1	w	0	w
0	1	1	0	x		
0	1	1	1	x'	1	x'
1	0	0	0	y'		
1	0	1	0	yz'	$yz'+yz=y$	yz
1	0	1	1	yz		
1	1	0	1	$y'z$		
1	1	1	0	y	$y+y'z=y+z$	$y'z+y'z'=y'$
1	1	1	1	$y'z'$		


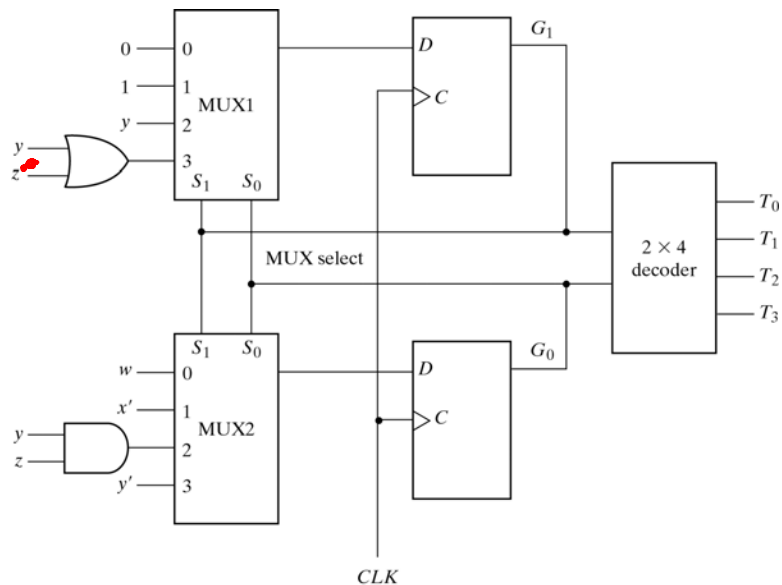


Fig. 8-20 Control Implementation with Multiplexers

Counting the number of 1's

 - The system counts the number of 1's in R1, and set R2 accordingly.
- The bits in R1 are shifted one at a time, checking if the shifted out bit is 1 or 0, and incrementing R2
- Z is a signal to indicate if R1 contains all 0's or not.
- E is the output of the flip-flop (the shifted out bit).



© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

Fig. 8-21 ASM Chart for Count-of-Ones Circuit

E could not be checked in the same block as T2 since the shift to E will not happen until the end of the cycle.

 


Fig. 8-21 ASM Chart for Count-of-Ones Circuit

© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.


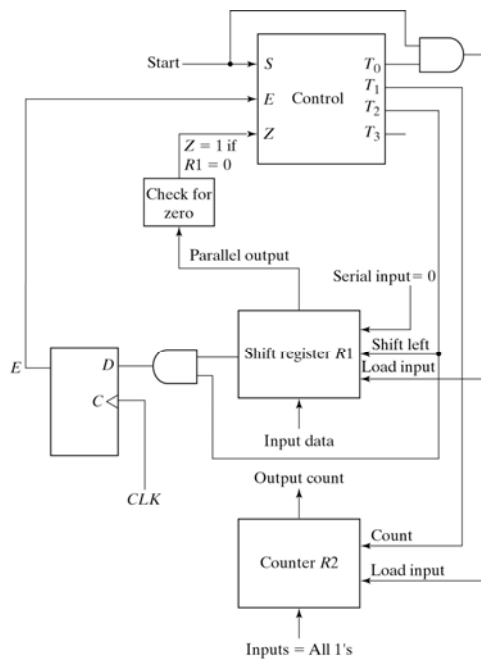


Fig. 8-22 Block Diagram for Count-of-Ones

© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

Control (counting of 1's)

Present State		Next State		Conditions	MUX inputs	
G1	G0	G1	G0		MUX1	MUX2
0	0	0	0	S'		
0	0	0	1	S	0	S
0	1	0	0	Z		
0	1	1	0	Z'	Z'	0
1	0	1	1		1	1
1	1	1	0	E'		
1	1	0	1	E	E'	E

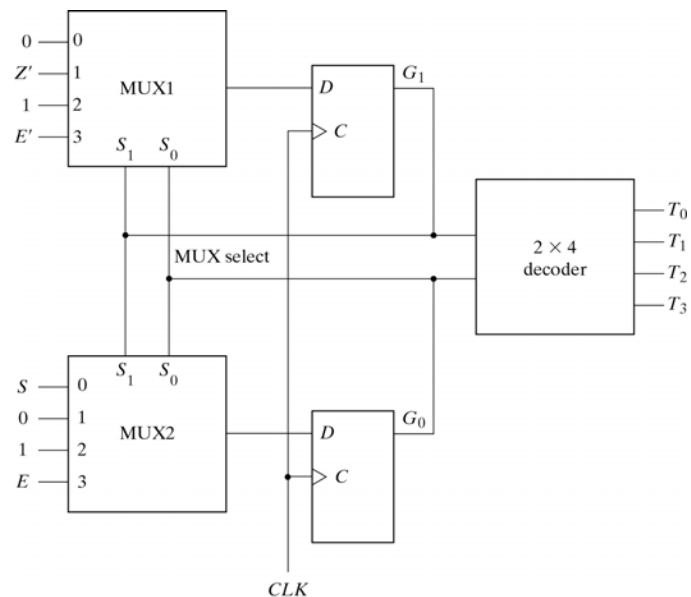

 


Fig. P8-10 Control State Diagram for Problems 8-10 and 8-11

© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

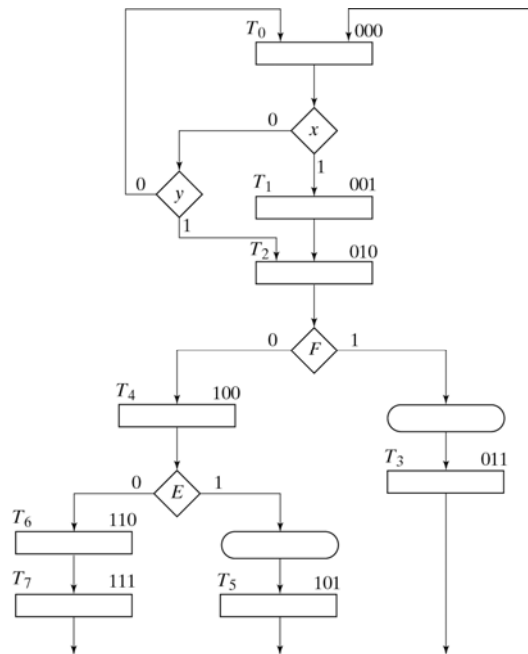


Fig. P8-20 ASM Chart for Problems 8-20

© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.