

Digital Logic Design

Hazards and Glitches


Fall 2007

CSE3201

1

Hazards and Glitches

- Gates do not change their outputs instantaneously after changing the input.
- A propagation delay that depends on the gate, V_{dd} , ...

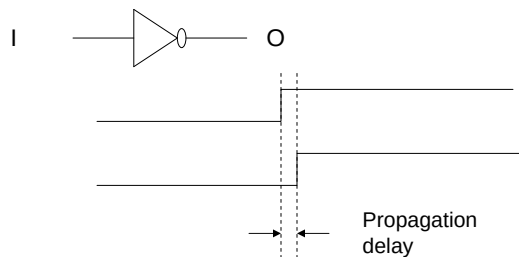


Fall 2007

CSE3201

2

Hazards

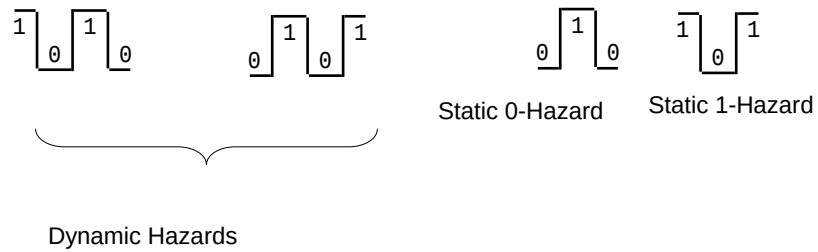


Fall 2007

CSE3201

3

Static Hazards -- Example

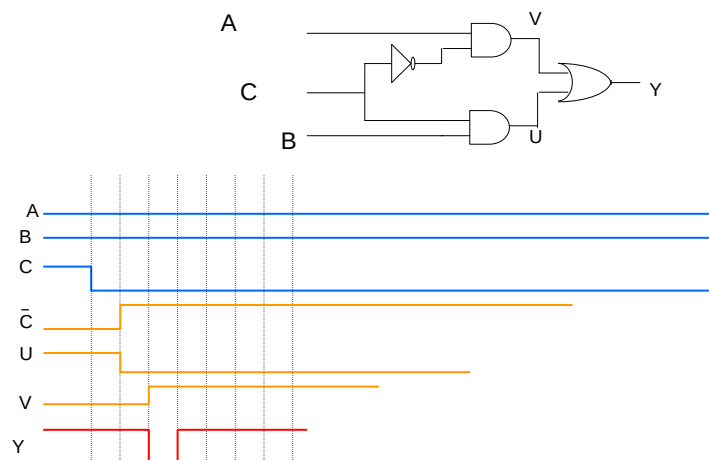


Fall 2007

CSE3201

4

Static Hazard -- Example

$\begin{smallmatrix} C \\ \backslash AB \end{smallmatrix}$	00	01	11	10
0	0	0	1	1
1	0	1	1	0

 


Fall 2007

CSE3201

5

Dynamic Hazard

 

Fall 2007

CSE3201

6

Hazards Free Circuits

- For static hazards, we can use K-map and be sure that adjacent 1's are covered by a minterm.
- Not minimum anymore
- No static hazards does not mean no dynamic hazards.
- Best is to design the circuit as a 2-level circuit