

## A Cubical technique for Minimization

- The initial specification of the function is given in the form of implicants (not necessarily prime or minterms).
- Use the intersection ( $*$  operation) as defined earlier
- First, find all the prime implicants
- Find the essential prime implicants
- Find minimum coverage

Week3

29

## A Cubical technique for Minimization

- Let  $A=\{A_1, A_2, \dots, A_n\}, B=\{B_1, B_2, \dots, B_n\}$  be two implicants
- Find  $C=A * B$ 
  - $C = \phi$  if  $A_i * B_i = \phi$  for more than one  $i$
  - $c_i = A_i * B_i$  where  $A_i * B_i \neq \phi$ , and  $c_i = x$  if  $A_i * B_i = \phi$

$\cap$	0	1	X
0	0	$\phi$	0
1	$\phi$	1	1
X	0	1	x

Week3

30

## A Cubical technique for Minimization cont.

- Find new cubes that are not included in the existing cubes.
- $G^{k+1} = c_i * c_j$  for all  $c_i, c_j$  in  $C^k$
- $C^{k+1} = C^k \cup G^{k+1}$  - redundant cubes
- Repeat until  $C^{k+1} = C^k$ , then we have the set of all prime implicants

Week3

31

## Example

Week3

32

## Finding Essential Prime Implicants

Define the # operation

# operation returns the part of A that is not covered by B

$C = A \# B$  such that

$C = A$  if  $A_i \# B_i = \phi$  for some  $i$

$C = \phi$  if  $A_i \# B_i = \varepsilon$  for all  $i$

Otherwise  $C = \cup_i (A_1, A_2, \dots, B_i', \dots, A_n)$   
where the union is for all  $i$  for which  $A_i = x$   
and  $B_i \neq x$ .

	0	1	x
0	$\varepsilon$	$\phi$	$\varepsilon$
1	$\phi$	$\varepsilon$	$\varepsilon$
X	1	0	$\varepsilon$

$A_i \# B_i$

Week3

33

## Finding Essentials Prime Implicants

- Let  $P$  be the set of all prime implicants, and  $DC$  is the set of all don't care.
- Let  $p_i$  denote one prime implicant
- $P_i$  is an essential prime implicant if

$$p^i \# (P - p^i) \# DC \neq \phi$$

- The meaning of  $\#$  is that the # operation is applied successively to each prime implicant in  $P$ , if  $P = \{p^1, p^2, p^3, p^4\}$  and  $DC = \{d^1, d^2\}$  then we evaluate

$$(((p^3 \# p^1) \# p^2) \# p^4) \# d^1) \# d^2$$

Week3

34

## Finding Essentials Prime Implicants

- Example
- Consider the set {x01x, x101, 01x1, xx10}

Week3

35

## Complete Procedure


- Let  $C^0$  = set of initial cover of  $f$  and DC
- Find all prime implicants of  $C^0 = P$
- Find the essential prime implicants. If that set covers all the vertices of  $f$  this is the minimum cover
- Delete any non essential  $p^i$  that is more expensive than other prime implicant  $p^j$  if  $p^i \neq DC$  #  $p^j = \phi$
- Choose the lowest-cost prime implicants to cover the remaining vertices of  $f$ . Use branching

Week3

36

# NAD and NOR Implementation


- Universal gate

 

Week3

37

## NAND Gate

 


2 graphic symbols for NAND gate

Week3

38

## 2-Level Implementation

- Start with sum of product  $F=AB+CD$

 

Week3

39

## NAND Implementation

- Express the function in sum of products
- Replace every AND by a NAND
- Replace the OR by Invert-OR
- If a single element is an input to the OR invert it.
- Change invert-OR to AND-invert
- Example on 3 variables

Week3

40

## Multilevel NAND Circuits

- Convert all AND gates to NAND gates with AND-invert symbols
- Convert all OR gates to NAND gates with invert-OR symbols
- Check all the bubbles in the diagram, for every bubble that is not compensated by another bubble on the same line, add an inverter (or compliment the input literal)

Week3

41


## NOR Implementation

Week3

42
 
## Wired Logic

- Wired AND in open collector TTL
- Wired-OR in ECL gates



Wired-AND in TTL

Week3

43

## AND-OR-INVERT AOI


- In CMOS, and in most other logic families, the simplest gates are inverters, then NAND and NOR gates.
- It is typically not possible to design a noninverting gate with less transistors than an inverting gate.
- CMOS circuits can perform two levels of logic with just a single level of transistors. (AOI gate).
- The speed and other electrical characteristics of a CMOS AOI or OAI gate are quite comparable to those of a single CMOS NAND or NOR.

Week3

44



## AOI

 

Week3

45

## AOI Gates

- If you implement the complement of the function in sum of products it results in AOI circuit

Week3

46

## Other 2-level Implementation

- Consider the function  
 $F = x'y'z' + xyz'$
- Take the complement  
 $F' = x'y + xy' + z$
- You can implement it as AOI using  $F'$
- Change it to NAND-AND by moving the bubble from the output of the OR to its inputs (and changing it to AND)  
NAND-AND implementation

		Y	
1	0	0	0
0	0	0	1
		Z	

Week3

47

## Other 2-level Implementation



- Using product of sums
- $F = z'(x+y')(x'+y)$ , OR we can say
- $F' = [(x'+y'+z)(x+y+z)]$
- We can implement the above equation using OR and NAND (OR-NAND implementation).
- Then we can move the bubble of the NAND to its inputs and changing it to OR (NOR-OR implementation)

Week3

48

# EX-OR



- $x \oplus y = x'y + y'x$

  

Week3

49

- 3 and 4 inout EX-OR Parity

  

Week3

50

# HDL

- Can be used to represent logic diagram, Boolean expressions, and finite state machine representation.
- Used to document digital systems
- Used in simulation and synthesis
- 2 main languages, Verilog, and VHDL

Week3

51

# Verilog

- C-like syntax
- Case sensitive, // for comments

```
module simpl_circuit(A,B,C,x,y);  
    input A,B,C;  
    output x,y;  
    wire e;  
    and g1(e,A,B);  
    not g2(y,c);  
    or g3(x,e,y);  
endmodule
```

Week3

52

# Verilog

- We can introduce delay

```
module smpl_circuit(A,B,C,x,y);  
    input A,B,C;  
    output x,y;  
    wire e;  
    and #(30) g1(e,A,B);  
    not #(20) g2(y,c);  
    or #(10) g3(x,e,y);  
endmodule
```

Week3

53

# Verilog

```
// Behavioral Model of a Nand gate  
// By Dan Hyde, August 9, 1995  
module NAND(in1, in2, out);  
    input in1, in2;  
    output out;  
    // continuous assign statement  
    assign out = ~(in1 & in2);  
endmodule
```

- The continuous assignment statement is used to model **combinational circuits** where the outputs change when one wiggles the input.

Week3

54

# Verilog

```
module AND(in1, in2, out);  
  // Structural model of AND gate from two NANDS  
  input in1, in2;  
  output out;  
  wire w1;  
  // two instantiations of the module NAND  
  NAND NAND1(in1, in2, w1);  
  NAND NAND2(w1, w1, out);  
endmodule
```

Week3

55

# Testing

```
module test_AND;  
  // High level module to test the two other modules  
  reg a, b;  
  wire x,y;  
  Circuit_with_delay cwd(A,B,C,x,y);  
  initial  
    begin // Test data  
      A=1'b0; B=1'b0; C=1'b0;  
      #100 A=1'b1; B=1'b1; C=1'b1;  
      #100 $finish;  
    end  
endmodule  
Module circuit_with_delay(A,B,C,x,y);  
  input A,B,C;  
  output x,y;  
  wire e;  
  and #(30) g1(e,A,B);  
  not #(20) g2(y,c);  
  or #(10) g3(x,e,y);  
endmodule
```

Week3

56

# User Defined Primitives

```
//User defined primitive(UDP)
primitive crcctp(x,A,B,C);
    output x;
    input A,B,C;
//Now the truth table
    table
//  A      B      C      :      x
    0      0      0      :      1;
    0      0      1      :      0;
    0      1      0      :      1;
    0      1      1      :      0;
    1      0      0      :      1;
    1      0      1      :      0;
    1      1      0      :      1;
    1      1      1      :      1;
    endtable
Endprimitive
module abcdef;
    reg x,y,z;
    wire w;
    crcctp(w,x,y,z);
endmodule
```

Week3

57