

York University  
Dept. of Computer Science and Engineering  
Digital Logic Design  
CSE3201  
Lab 6

***Objective***

In this lab, you will design a more complicated circuit that consists of more than one part.

***Problem***

Design a simple calculator that can multiply two single digit numbers, each digit is 0-9 and entered as a 4-bit binary number. The result is displayed on the 7-segment display. If any of the 2 numbers is greater than 9, the 7-segment display should be set to “E”

***Prep work***

Draw the circuit, and write the Verilog code. The circuit and the code should be **typed**

***In the lab***

Implement the circuit and demonstrate it to the TA