

# CSE4210

## Architecture and Hardware for DSP

### Lecture 1 Retiming


1

## Introduction

- Retiming is a transformation technique that is used to change the locations of delay elements in a circuit without changing its functionality.
- Can be used to reduce the number of registers, or the clock cycle
- Could be considered as a generalization of the pipelining technique studies earlier


2

# Retiming

 

3

# Introduction

 

4

## Definitions

- Mapping  $G$  to  $G_r$
- A retiming solution is a value  $r(V)$  for every node in the graph.
- $w(e)$  is the original weight of the edge  $e$
- $w_r(e)$  is the weight in the retimed graph
- Edge  $e$  is from  $U \rightarrow V$   
$$w_r(e) = w(e) + r(V) - r(U)$$
- A solution is feasible if all  $w_r \geq 0$
- For previous example,  $r(1)=r(3)=r(4)=0$ ,  $r(2)=-1$

5

## Definitions

- The weight of a path from  $a$  to  $b$  is  
$$w_r(p) = w(p) + r(b) - r(a)$$
- Retiming does not change the number of delays in a cycle.
- Retiming does not change iteration bound
- Adding a constant to all the  $r(V)$  produce the same circuit

6


## Solving Systems of Inequalities

- Draw the constraints graph
  - Draw node 1 to N from the graph + node N+1
  - For each inequality  $r_i - r_j \leq k$ , ( $k$  is integer) draw an edge from node  $j \rightarrow i$  with weight  $k$
  - For each node  $i=1,2,\dots,N$  draw an edge  $N+1 \rightarrow i$  with weight 0
- Solve
  - The system has a solution if the constraints graph has no negative cycle.
  - One solution is the min. length from node N+1 to  $i$

7

 
## Example

- 1
- $$r_1 - r_2 \leq 0$$
- $$r_3 - r_1 \leq 5$$
- $$r_4 - r_1 \leq 4$$
- $$r_4 - r_3 \leq -1$$
- $$r_3 - r_2 \leq 2$$



8

## Example

 

9

## Cutset Retiming

- **Cutset**: A set of edges if removed, the graph  $G$  is partitioned into 2 graphs  $G_1, G_2$ .
- Cutset retiming is done by adding  $k$  delays to all the edges in the cutset from  $G_1$  to  $G_2$ , and removing  $k$  delays from the edges from  $G_2$  to  $G_1$

$$- \min_{G_1 \xrightarrow{e} G_2} \{w(e)\} \leq k \leq \min_{G_2 \xrightarrow{e} G_1} \{w(e)\}$$


10

## Cutset Retiming

- Cutset retiming is a special case of retiming, where every node in  $G_1$  has a retiming value of  $J$ , and every node in  $G_2$  has a retiming value of  $J+K$  ( $J$  is unimportant).

11


## Cutset Retiming

 

Of course we should not have any negative delays after the transformation.


12

## Cutset

 

13

## Cutset

 


14

## Cutset Retiming

- Pipelining is a special case where there are no nodes from  $G_2$  to  $G_1$  (no loops).
- Cutset is combined with *slow-down*, where first an N-slow-down version of the graph is created by changing every D to ND, then retiming is used.
- With the N-slow-down version, the input is slowed down too (N-1 null operation or 0 samples must be interleaved with input data

15

## Example

 


Clock Cycle ?

16




100 stage lattice filter

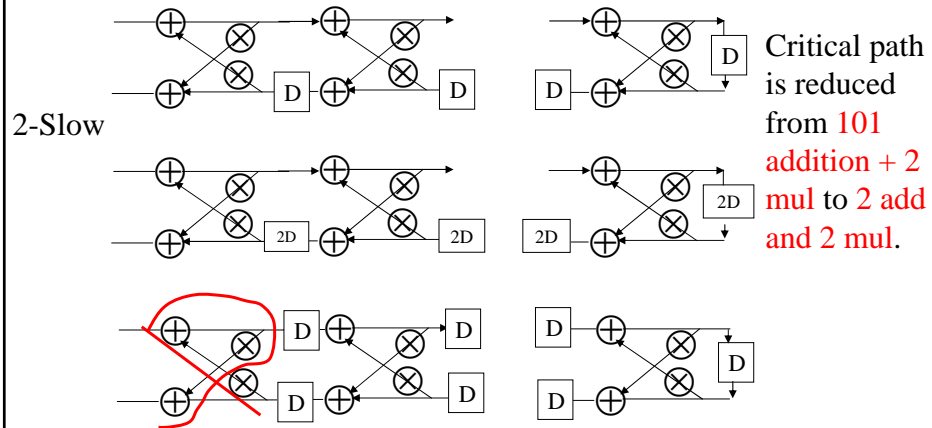


17

Example

 

18

$$T_{mul}=T_{add}=1$$

 

Time	Action	Time	Action	Action
1	$y(1)=ay(-1)+x(1)$	1	$y(1)=x(1)+w(0)$	$w(1)=ay(0)$
2		2	$y(2)=x(2)+w(1)$	$w(2)=ay(1)$
3	$y(2)=ay(0)+x(2)$	3	$y(3)=x(3)+w(2)$	$w(3)=ay(2)$
4		4	$y(4)=x(4)+w(3)$	$w(4)=ay(3)$
5	$y(3)=ay(1)+x(3)$	5	$y(5)=x(5)+w(4)$	$w(5)=ay(4)$
6		6	$y(6)=x(6)+w(5)$	$w(6)=ay(5)$
7	$y(4)=ay(2)+x(4)$	7	$y(7)=x(7)+w(6)$	$w(7)=ay(6)$
8				

## Example



ARE THESE  
EQUIVALENT?

## Retiming for Period Minimization

- We can use retiming to minimize the period (maximize the clock rate).
- The minimum period is the computation time of the critical path

$$\Phi(G) = \max\{t(p) : w(p) = 0\}$$

21

## Minimize Clock Period

- $W(U,V)$  is the minimum number of registers on any path from  $U \rightarrow V$
- $D(U,V)$  is the max. computation time among all paths from  $U \rightarrow V$  with weight  $W(U,V)$

$$W(U,V) = \min\{w(p) : p \text{ is a path from } U \text{ to } V\}$$

$$D(U,V) = \max\{w(p) : p \text{ is a path from } U \text{ to } V, \text{ and } w(p) = W(U,V)\}$$


22

## Minimize Clock Period

1. Let  $M = n t_{max}$ , where  $t_{max}$  is the max. computation time of any node,  $n$  = number of nodes
2. Form a new graph  $G'$  which is the same as  $G$  except the edge weights are replaced by  $w'(e) = Mw(e) - t(U)$  ( $e = U \rightarrow V$ )
3. Solve for all-pairs shortest path on  $G'$  ( $S_{UV}$ )
  1. If  $U \neq V$ , then  $W(U,V) = \lceil S_{UV}/M \rceil$  and  $D(U,V) = MW(U,V) - S_{UV} + t(V)$
  2. IF  $U=V$ ,  $W(U,V)=0$ ,  $D(U,V)=t(U)$

23

## Example $M = nt_{max} = 4 * 2 = 8$

 

$$S_{UV} = \begin{bmatrix} 12 & 5 & 7 & 15 \\ 7 & 12 & 14 & 22 \\ 5 & -2 & 12 & 20 \\ 5 & -2 & 12 & 20 \end{bmatrix}$$

24

## Example

$$S_{UV} = \begin{bmatrix} 12 & 5 & 7 & 15 \\ 7 & 12 & 14 & 22 \\ 5 & -2 & 12 & 20 \\ 5 & -2 & 12 & 20 \end{bmatrix}$$

$$W(U,V) = \begin{bmatrix} 0 & 1 & 1 & 2 \\ 1 & 0 & 2 & 3 \\ 1 & 0 & 0 & 3 \\ 1 & 0 & 2 & 0 \end{bmatrix}$$

$$\begin{cases} U \neq V & W(U,V) = \left\lceil \frac{S_{UV}}{M} \right\rceil, D(U,V) = MW(U,V) - S_{UV} + t(V) \\ U = V & W(U,V) = 0, D(U,V) = t(U) \end{cases} \quad D(U,V) = \begin{bmatrix} 1 & 4 & 3 & 3 \\ 2 & 1 & 4 & 4 \\ 4 & 3 & 2 & 6 \\ 4 & 3 & 6 & 2 \end{bmatrix}$$

25


## Minimize Clock Period

- After getting  $W(U,V), D(U,V)$  construct the following set of constraints
- Feasibility constraints  $r(U) - r(V) \leq w(e)$  for every edge in  $G$
- Critical path constraint  $r(U) - r(V) \leq W(U,V) - 1$  for all nodes  $U, V$  in  $G$  such that  $D(U,V) > c$  (cycle time).
- Solve to get  $r(.)$  (retiming values)  
 $w_r(p) = w(p) + r(b) - r(a)$

26

## Example

$$c=3$$

 

### Feasibility Constraints

$$\begin{aligned} r(1)-r(2) &\leq 1 \\ r(1)-r(4) &\leq 2 \\ r(2)-r(1) &\leq 1 \\ r(1)-r(2) &\leq 1 \\ r(3)-r(2) &\leq 0 \\ r(4)-r(2) &\leq 0 \end{aligned}$$

$$W(U,V) = \begin{bmatrix} 0 & 1 & 1 & 2 \\ 1 & 0 & 2 & 3 \\ 1 & 0 & 0 & 3 \\ 1 & 0 & 2 & 0 \end{bmatrix}$$

$$D(U,V) = \begin{bmatrix} 1 & \underline{4} & 3 & 3 \\ 2 & 1 & \underline{4} & \underline{4} \\ \underline{4} & 3 & 2 & \underline{6} \\ \underline{4} & 3 & \underline{6} & 2 \end{bmatrix}$$

### Critical Path Constraints

$$\begin{aligned} r(1)-r(2) &\leq 0 \\ r(2)-r(3) &\leq 1 \\ r(2)-r(4) &\leq 2 \\ r(3)-r(1) &\leq 0 \\ r(4)-r(1) &\leq 0 \\ r(4)-r(3) &\leq 1 \end{aligned}$$

27

## Retiming for Register Minimization

- The number of registers required to implement the output edges of node  $v$

$$R_V = \max_{V \xrightarrow{e} ?} \{W_r(e)\}$$

- Minimize**

$$COST = \sum R_V$$

$$R_V \geq w_r(e) \text{ for all } V \text{ and all edges } V \xrightarrow{e} ?$$

$$r(U) - r(V) \leq w(e) \text{ for every edge } U \xrightarrow{e} V$$

$$r(U) - r(V) \leq W(U,V) - 1 \text{ for every vertices } U, V \text{ such that } D(U,V) > c$$

28