

# Digital Logic Design

## Week 3 Gate-Level Minimization

Week3

1

## Outline

- The Map Method
- 2,3,4 variable maps
- 5 and 6 variable maps (very briefly)
- Product of sums simplification
- Don't Care conditions
- NAND and NOR implementation
- Other 2-level implementation
- Hardware Description language (HDL)

Week3

2

# The Map Method

- After constructing the map. We mark the squares whose minterms.
- Any two adjacent squares in the map differ by only one variable, primes in one square and unprimed in the other.
- The sum of the elements in these 2 squares, can be simplified to an and gates that does not contain that literal.
- The more adjacent squares we combine them together, the simple the term will be.

Week3

3

## 2-variable map

Y	0	1
X		
0	$m_0$	$m_1$
1	$m_2$	$m_3$

Week3

4

# 3-variable map

		y			
		00	01	11	10
x	yz	00	01	11	10
	x'y'z'	x'y'z	x'yz	x'yz'	
	m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>	
	xy'z'	xy'z	xyz	xyz'	
	m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub>	m <sub>6</sub>	
		Z			

Week3

5

# 3-variable map

$$F = X'Z + X'Y + XY'Z + YZ$$

		y			
		00	01	11	10
x	yz	00	01	11	10
	x	1	1	1	
	x	1	1		
		Z			

$$F = Z + X'Y$$

Week3

6

# 4-variable map

		Y																							
		yz																							
		00	01	11	10																				
W	wx	<table border="1" style="width: 100%; height: 100%;"> <tr> <td style="text-align: center;">00</td> <td style="text-align: center;"><math>w'x'y'z'</math> <math>m_0</math></td> <td style="text-align: center;"><math>w'x'y'z</math> <math>m_1</math></td> <td style="text-align: center;"><math>w'x'yz</math> <math>m_3</math></td> <td style="text-align: center;"><math>w'x'yz'</math> <math>m_2</math></td> </tr> <tr> <td style="text-align: center;">01</td> <td style="text-align: center;"><math>w'xy'z'</math> <math>m_4</math></td> <td style="text-align: center;"><math>w'xy'z</math> <math>m_5</math></td> <td style="text-align: center;"><math>w'xyz</math> <math>m_7</math></td> <td style="text-align: center;"><math>w'xyz'</math> <math>m_6</math></td> </tr> <tr> <td style="text-align: center;">11</td> <td style="text-align: center;"><math>wxy'z'</math> <math>m_{12}</math></td> <td style="text-align: center;"><math>wxy'z</math> <math>m_{13}</math></td> <td style="text-align: center;"><math>wxyz'</math> <math>m_{15}</math></td> <td style="text-align: center;"><math>wxyz</math> <math>m_{14}</math></td> </tr> <tr> <td style="text-align: center;">10</td> <td style="text-align: center;"><math>wx'y'z'</math> <math>m_8</math></td> <td style="text-align: center;"><math>wx'y'z</math> <math>m_9</math></td> <td style="text-align: center;"><math>wx'yz</math> <math>m_{11}</math></td> <td style="text-align: center;"><math>wx'yz'</math> <math>m_{10}</math></td> </tr> </table>				00	$w'x'y'z'$ $m_0$	$w'x'y'z$ $m_1$	$w'x'yz$ $m_3$	$w'x'yz'$ $m_2$	01	$w'xy'z'$ $m_4$	$w'xy'z$ $m_5$	$w'xyz$ $m_7$	$w'xyz'$ $m_6$	11	$wxy'z'$ $m_{12}$	$wxy'z$ $m_{13}$	$wxyz'$ $m_{15}$	$wxyz$ $m_{14}$	10	$wx'y'z'$ $m_8$	$wx'y'z$ $m_9$	$wx'yz$ $m_{11}$	$wx'yz'$ $m_{10}$
	00					$w'x'y'z'$ $m_0$	$w'x'y'z$ $m_1$	$w'x'yz$ $m_3$	$w'x'yz'$ $m_2$																
	01					$w'xy'z'$ $m_4$	$w'xy'z$ $m_5$	$w'xyz$ $m_7$	$w'xyz'$ $m_6$																
	11					$wxy'z'$ $m_{12}$	$wxy'z$ $m_{13}$	$wxyz'$ $m_{15}$	$wxyz$ $m_{14}$																
10	$wx'y'z'$ $m_8$	$wx'y'z$ $m_9$	$wx'yz$ $m_{11}$	$wx'yz'$ $m_{10}$																					
00																									
01																									
10																									
		Z																							

Week3

7

# 4-variable map

		Y																							
		yz																							
		00	01	11	10																				
W	wx	<table border="1" style="width: 100%; height: 100%;"> <tr> <td style="text-align: center;">00</td> <td style="text-align: center;"><b>1</b></td> <td style="text-align: center;"><b>1</b></td> <td></td> <td style="text-align: center;"><b>1</b></td> </tr> <tr> <td style="text-align: center;">01</td> <td style="text-align: center;"><b>1</b></td> <td style="text-align: center;"><b>1</b></td> <td></td> <td style="text-align: center;"><b>1</b></td> </tr> <tr> <td style="text-align: center;">11</td> <td style="text-align: center;"><b>1</b></td> <td style="text-align: center;"><b>1</b></td> <td></td> <td style="text-align: center;"><b>1</b></td> </tr> <tr> <td style="text-align: center;">10</td> <td style="text-align: center;"><b>1</b></td> <td style="text-align: center;"><b>1</b></td> <td></td> <td></td> </tr> </table>				00	<b>1</b>	<b>1</b>		<b>1</b>	01	<b>1</b>	<b>1</b>		<b>1</b>	11	<b>1</b>	<b>1</b>		<b>1</b>	10	<b>1</b>	<b>1</b>		
	00					<b>1</b>	<b>1</b>		<b>1</b>																
	01					<b>1</b>	<b>1</b>		<b>1</b>																
	11					<b>1</b>	<b>1</b>		<b>1</b>																
10	<b>1</b>	<b>1</b>																							
00																									
01																									
10																									
		Z																							

Week3

8

## 5-Variable Map

- Mention an example for 5 and 6 very briefly,
- Too complicated

Week3

9

## Prime Implicants

- **prime Implicant:** is a product term obtained by combining together the maximum possible number of adjacent squares in the map.
- **Essential prime implicant:** if a minterm in the map is covered by only one prime implicant, this prime implicant is called an essential prime implicant.

Week3

10

# Prime Implicant

- The procedure of finding the simplified expression from the map is as follows:
  1. First, determine all the essential prime implicants.
  2. The simplified expression is obtained by combining all the essential prime implicants
  3. After that add other prime implicants that may be needed to cover any remaining minterms that was not covered by essential prime implicants.

Week3

11

# Example

$$F = \Sigma(0,2,3,5,7,8,9,10,11,13,15)$$

		Y				
		00	01	11	10	
W	yz					
	wx					
	00	<b>1</b>		<b>1</b>	<b>1</b>	X
	01		<b>1</b>	<b>1</b>		
11		<b>1</b>	<b>1</b>			
10	<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>		
		Z				

Week3

12

## Prime Implicant

- In the previous map, there are 2 essential prime implicant ( $B'D'$  the only way to cover  $m_0$ , and  $BD$  the only way to cover  $m_9$ ).
- Add other prime implicant to cover minterms  $m_3$ ,  $m_9$ , and  $m_{11}$ .
- Minterm  $m_3$  can be covered by either  $CD$  or  $B'C$ . minterm  $m_9$  can be covered by either  $AD$  or  $AB'$ . While minterm  $m_{11}$  is covered by any one of the 4 prime implicant.
- There are 4 possible way to describe this function, all of them include both  $BD$  and  $B'D'$  and we can add  $(CD+AD)$ ,  $(CD+AB')$ ,  $B'C+AD$ , or  $(B'C+AB')$ .

Week3

13

## Product of Sum Simplification

- $F=A+DB+C'A$
- Using maxterm
- $F=(A+D)(A+B)$
- $F=A+AB+DA+DB$
- O.K.

Week3

14

				B	
		yz			
		00	01	11	10
AB					
	00	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>
	01	<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>
A	11	<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>
	10	<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>
				C	

Week3

15


## Don't Care Conditions

- Used as 1 or zero to simplify the design



# NAND and NOR Implementation

- Universal gate

 

Week3

17

# NAND Gate



AND-invert

Invert-OR


2 graphic symbols for NAND gate

Week3

18

## 2-Level Implementation

- Start with sum of product  $F=AB+CD$

 

Week3

19

## NAND Implementation

- Express the function in sum of products
- Replace every AND by a NAND
- Replace the OR by Invert-OR
- If a single element is an input to the OR invert it.
- Change invert-OR to AND-invert
- Example on 3 variables

Week3

20

## Multilevel NAND Circuits

- Convert all AND gates to NAND gates with AND-invert symbols
- Convert all OR gates to NAND gates with invert-OR symbols
- Check all the bubbles in the diagram, for every bubble that is not compensated by another bubble on the same line, add an inverter (or compliment the input literal)

Week3

21


## NOR Implementation

Week3

22
 
## Wired Logic

- Wired AND in open collector TTL
- Wired-OR in ECL gates



Wired-AND in TTL

Week3

23

## AND-OR-INVERT AOI

- In CMOS, and in most other logic families, the simplest gates are inverters, then NAND and NOR gates.
- It is typically not possible to design a noninverting gate with less transistors than an inverting gate.
- CMOS circuits can perform two levels of logic with just a single level of transistors. (AOI gate).
- The speed and other electrical characteristics of a CMOS AOI or OAI gate is quite comparable to those of a single CMOS NAND or NOR.

Week3

24

## AOI Gates

- If you implement the complement of the function in sum of products it results in AOI circuit

Week3

25

## Other 2-level Implementation

- Consider the function  
 $F = x'y'z' + zyz'$
- Take the complement  
 $F' = x'y + xy' + z$
- You can implement it as AOI using  $F'$
- Change it to NAND-AND by moving the bubble from the output of the OR to its inputs (and changing it to AND)  
NAND-AND implementation

					Y
1	0	0	0		
0	0	0	1		
					Z

Week3

26

## Other 2-level Implementation



- Using product of sums
- $F = z'(x+y')(x'+y)$ , OR we can say
- $F' = [(x'+y'+z)(x+y+z)]$
- We can implement the above equation using OR and NAND (OR-NAND implementation).
- Then we can move the bubble of the NAND to its inputs and changing it to OR (NOR-OR implementation)

Week3

27

## EX-OR

- $x \oplus y = x'y + y'x$

  

Week3

28

- 3 and 4 inout EX-OR Parity



Week3

29

## HDL

- Can be used to represent logic diagram, Boolean expressions, and finite state machine representation.
- Used to document digital systems
- Used in simulation and synthesis
- 2 main languages, Verilog, and VHDL

Week3

30

# Verilog

- C-like syntax
- Case sensitive, // for comments

```
module simpl_circuit(A,B,C,x,y);  
    input A,B,C;  
    output x,y;  
    wire e;  
    and g1(e,A,B);  
    not g2(y,c);  
    or g3(x,e,y);  
endmodule
```

Week3

31

# Verilog

- We can introduce delay

```
module simpl_circuit(A,B,C,x,y);  
    input A,B,C;  
    output x,y;  
    wire e;  
    and #(30) g1(e,A,B);  
    not #(20) g2(y,c);  
    or #(10) g3(x,e,y);  
endmodule
```

Week3

32



# Verilog

```
// Behavioral Model of a Nand gate
// By Dan Hyde, August 9, 1995
module NAND(in1, in2, out);
input in1, in2;
output out;
// continuous assign statement
assign out = ~(in1 & in2);
endmodule
```

- The continuous assignment statement is used to model **combinational circuits** where the outputs change when one wiggles the input.

Week3

33

# Verilog

```
module AND(in1, in2, out);
// Structural model of AND gate from two NANDS
input in1, in2;
output out;
wire w1;
// two instantiations of the module NAND
NAND NAND1(in1, in2, w1);
NAND NAND2(w1, w1, out);
endmodule
```

Week3

34

# Testing

```
module test_AND;
// High level module to test the two other modules
reg a, b;
wire x,y;
Circuit_with_delay cwd(A,B,C,x,y);
initial
begin // Test data
A=1'b0; B=1'b0; C=1'b0;
#100 A=1'b1; B=1'b1; C=1'b1;
#100 $finish;
end
endmodule
Module circuit_with_delay(A,B,C,x,y);
input A,B,C;
output x,y;
wire e;
and #(30) g1(e,A,B);
not #(20) g2(y,c);
or #(10) g3(x,e,y);
endmodule
```

Week3

35

# User Defined Primitives

```
//User defined primitive(UDP)
primitive crctp(x,A,B,C);
output x;
input A,B,C;
//Now the truth table
table
// A B C : x
0 0 0 : 1;
0 0 1 : 0;
0 1 0 : 1;
0 1 1 : 0;
1 0 0 : 1;
1 0 1 : 0;
1 1 0 : 1;
1 1 1 : 1;
endtable
Endprimitive
module abcdeE;
reg x,y,z;
wire w;
crctp(w,x,y,z);
endmodule
```

Week3

36