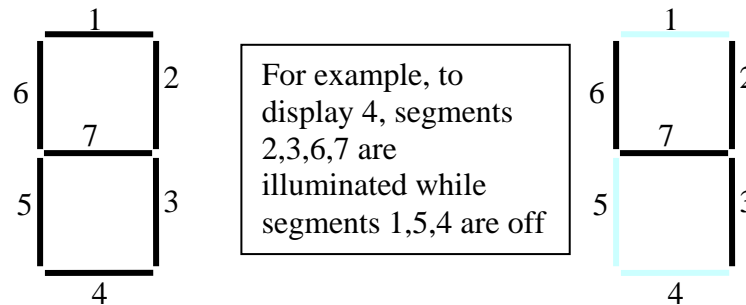


Dept. of Computer Science and Engineering  
CSE3201 – Digital Logic Design  
Lab 2

This lab is to get you acquainted with the design of a simple combinational circuit.

Design a circuit that display on one of the seven segments displays the binary value represented by the max of the two binary number represented by the 2 sets of switches SW0 to SW2, and SW3 to SW5.

For example if SW2 SW1 SW0 are 100 (4), and SW5 SW4 SW3 are 011 (3) the 7-segment display should display the number 4 ( $4 > 3$ ).



The seven segment display consists of 7 LEDs as shown in the above figure, the different LEDs are switched on and off to represent a certain number, so for example to represent the number 4, LEDs number 2,3,6 and 7 are ON the rest are off.

Construct a truth table to show the relation between the switches and the LEDS here is a partial table

A	B	C	LED1	LED2	LED3	LED4	LED5	LED6	LED7
0	0	0							
0	0	1							
0	1	0							
0	1	1							
1	0	0	0	1	1	0	0	1	1
1	0	1							
1	1	0							
1	1	1							

Complete the table to find the relation between the values of A,B, and C and the segments.

Using any technique, implement this circuit and download it on the D2 board

LED1 = function(SW2, SW1, SW0)

**Note** that a segment is illuminated by driving it to logic 0

***Pre-Lab Work***

Complete your design using Verilog, show the program to the TA before starting

***Lab report***

See the guidelines for the lab report on the Lab section of the course web page