


Digital Logic Design

CMOS

Fall 2011

CSE3201

MOS

 

Silicon Si (group IV) forms a covalent bonds with for adjacent atoms (3-D crystals).

All of its valence electrons (4) are involved in chemical bonds -- poor conductor


Conductivity can be raised by introducing a small amount of impurities (dopants)

Fall 2011

CSE3201

MOS

n-type

 

Fall 2011


CSE3201

A group V dopant such as Arsenic has 5 valence electrons, it replaces an Si atom in the lattice and bonds to 4 neighbors.

The 5th valence electron is loosely bound to the arsenic atom. Thermal vibration at room temperature is sufficient to set the electron free to move leaving a positively charged As⁺

MOS

p-type

 

Fall 2011

CSE3201

A group III dopant such as Boron has 3 valence electrons, it replaces an Si atom in the lattice and bonds to 4 neighbors.

Boron can borrow an electron from a neighboring Si atom, which can borrow an electron from a neighboring atom and so on, the hole (+) can move round.


p-n junction




Fall 2011

CSE3201

MOSFET Transistors

 

n-MOS

 

Fall 2011



The body is generally grounded

The p-n junction in the source and drain are reverse-biased, if the gate is grounded, no current flows


If the gate is +ve enough, an electric field is created that attract electrons to the surface.

Electrons outnumber the holes, and a thin region under the gate **channel** is inverted to be n-type and current can flow

CSE3201

 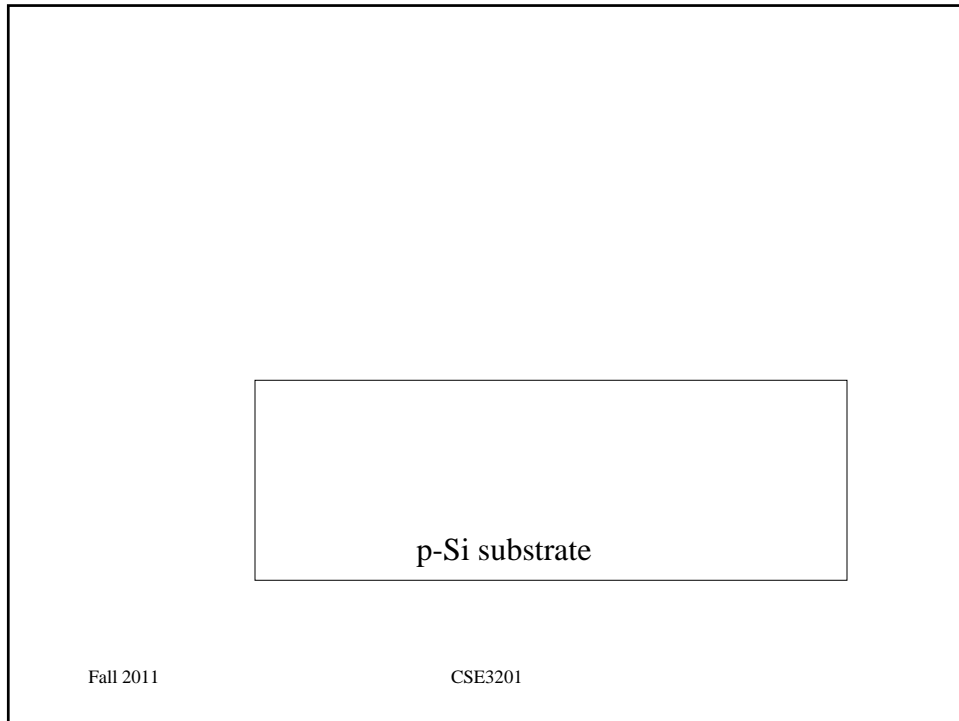

PR
SiO₂

 


p-Si substrate

Fall 2011

CSE3201



PR
SiO₂


 



p-Si substrate

Fall 2011

CSE3201

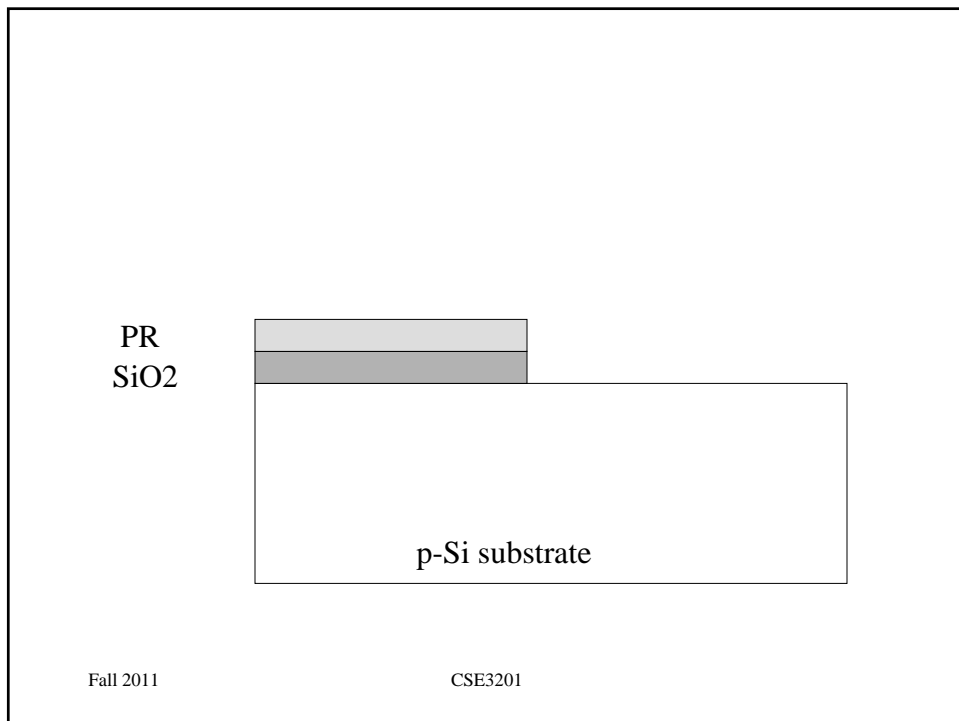 

 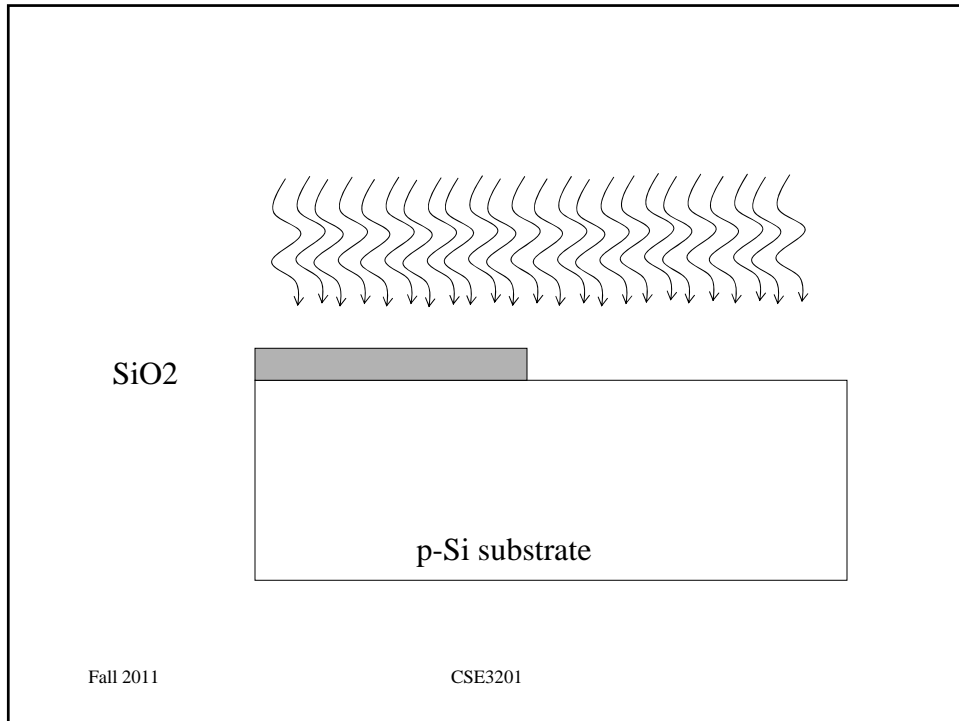


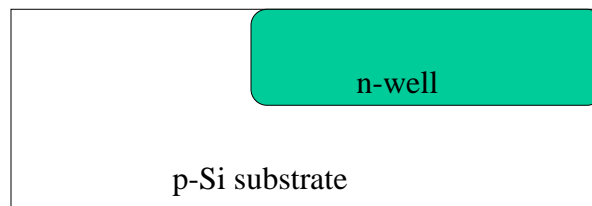

Fall 2011

CSE3201

Inverter

 


Fall 2011

CSE3201

N-Type MOS Transistor



- **Cut-off Region**
 - $V_{gs} - V_t \leq 0$
 - No current (I_{ds}) between drain and source
- **Linear (or Ohmic) Region**
 - $0 < V_{ds} < V_{gs} - V_t$
 - I_{ds} is a function of V_{gs} and V_{ds}
 - $I_{ds} = \beta * [(V_{gs} - V_t) * V_{ds} - V_{ds}^2 / 2]$
- **Saturation Region**
 - $0 < V_{gs} - V_t < V_{ds}$
 - I_{ds} is independent of V_{ds}
 - $I_{ds} = (\beta/2) * (V_{gs} - V_t)^2$
 - β = process factor * (W/L)
- V_t : Threshold voltage, a function of materials, doping, insulator thickness, etc.

 

N-type MOS Transistor

Fall 2011

CSE3201

  


N-type MOS Transistor

Fall 2011

CSE3201

Inverter

 

Fall 2011

CSE3201

CMOS Circuits

- In general, CMOS circuits consists of 2 components, pull up network, and a pull down network.
- The pull up and pull down networks are duals, (**sufficient but not necessary condition**) to construct one from the other:
 - Exchange NFETS for PFETS and vice versa
 - Exchange series connections with parallel connections and vice versa
- The pull up (pull down) network represents the computations of the function's 1(0)-valued outputs.

Fall 2011

CSE3201


CMOS Circuits

- nMOS transistors pass a strong 0
 - But degraded or weak 1
- pMOS transistors pass a strong 1
 - But degraded or weak 0
- Therefore, nMOS transistors are best for the “pull-down” network

Fall 2011

CSE3201

CMOS Circuits

 


	Pull-up OFF	Pull-up ON
Pull-down OFF	Z (float)	1
Pull-down ON	0	X (crowbar)

Fall 2011

CSE3201


Inverter

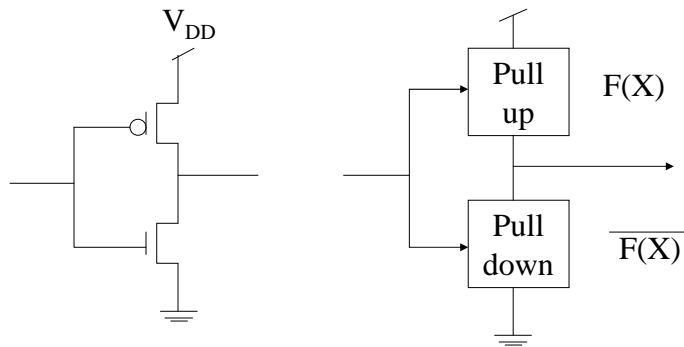

Fall 2011

CSE3201

NAND

 


What about AND?

Fall 2011

CSE3201

NOR

 

Fall 2011


CSE3201

Example

$$F = \overline{(A + B + C) \bullet D}$$

$$F = \overline{(A + B + C) + \overline{D}}$$

$$\overline{F} = (A + B + C) \bullet D$$

 

Fall 2011

CSE3201

Example


$$F + AB + C + \overline{D}E$$

Fall 2011

CSE3201


Transmission Gates

- nMOS transistors pass '0' well, but '1' poorly ($V_{DD} - V_{TN}$)
- pMOS is the opposite low voltage is not '0' but $|V_{TP}|$

 


Fall 2011

CSE3201

 

Noise Margin

 - V_{IH} = minimum HIGH input voltage
- V_{IL} = maximum LOW input voltage
- V_{OH} = minimum HIGH output voltage
- V_{OL} = maximum LOW output voltage



$$NM_L = V_{IL} - V_{OL}$$

Why do we need margin?

Typical CMOS vs. TTL

TABLE 8-9 Input/output voltage levels (in volts) with $V_{DD} = V_{CC} = +5\text{ V}$.


Parameter	CMOS							TTL		
	4000B	74HC	74HCT	74AC	74ACT	74AHC	74AHCT	74	74LS	74AS
$V_{IH}(\text{min})$	3.5	3.5	2.0	3.5	2.0	3.85	2.0	2.0	2.0	2.0
$V_{IL}(\text{max})$	1.5	1.0	0.8	1.5	0.8	1.65	0.8	0.8	0.8	0.8
$V_{OH}(\text{min})$	4.95	4.9	4.9	4.9	4.9	4.4	3.15	2.4	2.7	2.7
$V_{OL}(\text{max})$	0.05	0.1	0.1	0.1	0.1	0.44	0.1	0.4	0.5	0.5
V_{NH}	1.45	1.4	2.9	1.4	2.9	0.55	1.15	0.4	0.7	0.7
V_{NL}	1.45	0.9	0.7	1.4	0.7	1.21	0.7	0.4	0.3	0.3

Fall 2011

CSE3201

Fan out


- I_{OLmax} = the max. current that the output can sink in the LOW state and still maintain an output voltage no greater than V_{OLmax} .

 

Fall 2011


CSE3201

 - I_{OHmax} the maximum current that the output can source in the HIGH state and still maintain an output voltage no less than V_{OHmin} .




Fan Out

- I_{IH} is the current that the device sinks with a logic "1" at the input (20 mA).
- I_{IL} is the current that the device can sink with a logic "0" at the input. (-0.1 mA)


 


Fall 2011

CSE3201

 

Fan Out

  

$$\text{Fan out} = \max \left(\frac{I_{OH \max}}{I_{IH}}, \frac{I_{OL \max}}{I_{IL}} \right)$$

Fall 2011

CSE3201


Practical Consideration

- What happens when you overload a CMOS
 - V_{OL} may increase beyond $V_{OL \max}$ **What is wrong with that?**
 - V_{OH} may drop beyond $V_{OH \min}$ **What is wrong with that?**
 - Output rise and fall times may increase (slower operation)
- What to do with *unused inputs*?
 - Never leave unconnected
 - Either tie them together, tie them HIGH or LOW

Fall 2011

CSE3201

Transition Time

 

Fall 2011

CSE3201


CMOS Dynamic Behavior

- When a MOS transistor switches from HIGH to LOW or vice versa, it discharges or charges a capacitor
- That depends on the time constant of the (dis)charging circuits
- Time constant $\tau = RC$

Fall 2011

CSE3201


HIGH to LOW

 

Fall 2011

CSE3201

LOW to HIGH

 

Fall 2011

CSE3201

What is R and C

- Manufacturers do not specify the transistor "ON" resistance.
- Could be estimated as follows (keep in mind it is voltage controlled resistance which is controlled by V_{gs})

$$R_{p(on)} = \frac{V_{DD} - V_{OH \min T}}{|I_{OH \max T}|} \qquad R_{n(on)} = \frac{V_{OL \max T}}{I_{OL \max T}}$$

Fall 2011

CSE3201

Current Spikes

- WHEN CMOS transistors switches between LOW and HIGH, current flows between VDD and ground through the partially ON p and n transistors, that is known as current spikes.
- Systems that use CMOS circuits require *decoupling capacitors* between VDD and ground at least one within an inch or so from each chip.

Fall 2011

CSE3201

The Design Process

