

Digital Logic Design

Combinational Design

CSE3201

Fall 2011

1

Outline

- Combinational Circuits
- Analysis Procedure
- Design Procedure
- Adders and multipliers
- Comparators
- Decoders and Encoders
- Multiplexers
- HDL For Combinational Circuits

CSE3201

Fall 2011

2

Combinational Circuits

- What is a combinational circuit?
- What is the difference between combinational and sequential circuits
- Implementation MSI and standard cells in ASIC

CSE3201

Fall 2011

3

Analysis Procedure


1. Label all gate outputs that are a function of input variables with arbitrary symbols. Find the Boolean function of these gates
2. Label all the gates that are functions of input variables and previously labeled gates with arbitrary symbols. Find the Boolean function of these gates.
3. Repeat step 3 until the outputs of all the gates are labeled
4. By repeated substitution of previously defined functions, obtain the output Boolean functions in terms of input variables (or truth table)

CSE3201

Fall 2011

4

Analysis Procedure

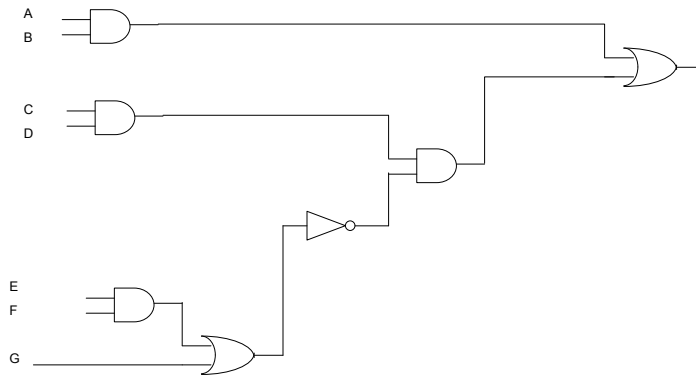

CSE3201

Fall 2011

5

Design Procedure

1. From the specification of the circuit. Determine the required number of input and output and assign a symbol to each.
 2. Derive the truth that defines the required relationship between inputs and outputs.
 3. Obtain the simplified Boolean expressions for each output as a function of the input variables.
 4. Draw the logic diagram and verify the correctness of the design.
- Example: BCD to Excess-3 Code Converter.


CSE3201

Fall 2011

6

Binary Adder-Subtractor

- Half adder: $S = x'y + xy'$, $C = xy$

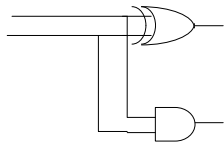

CSE3201

Fall 2011

7



Full Adder

x	y	z	s	c
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


CSE3201

Fall 2011

8

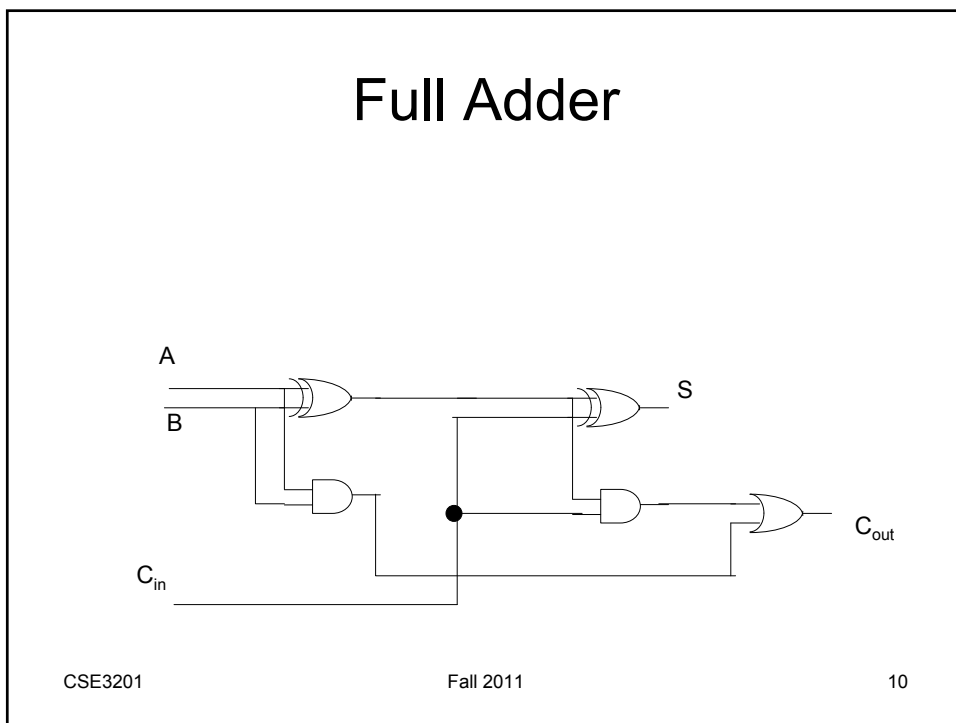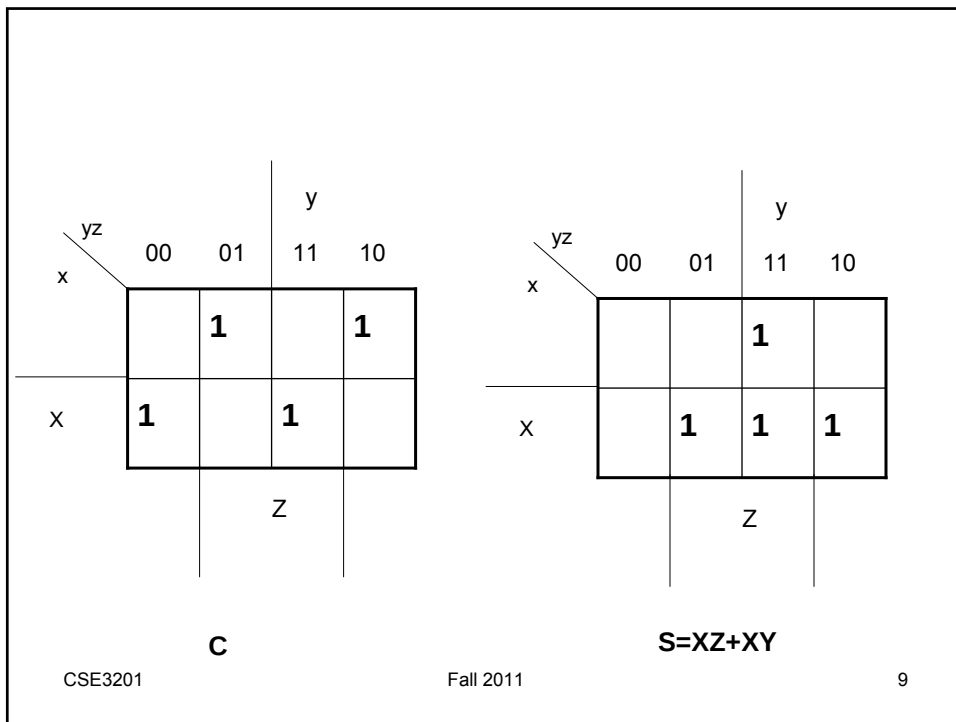

Binary Adder

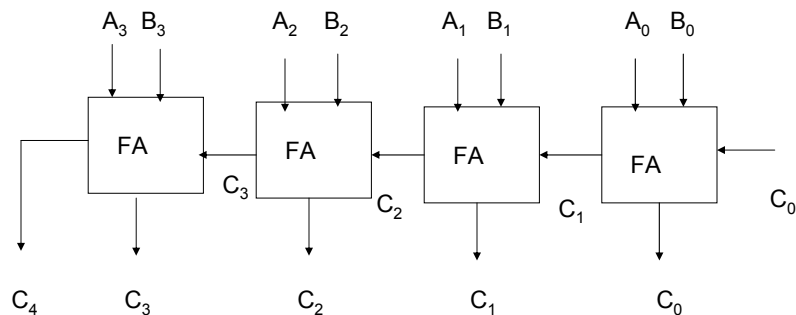

CSE3201

Fall 2011

11

Carry Propagation

- The value of s_i depends on the current A_i and B_i and C_i . C_i depends on A_{i-1} , and B_{i-1} , and so on.
- That means the carry propagates across all the digits in the two numbers to be added.
- Carry propagation time is a limiting factor on the speed of addition (basic operation in virtually everything).
- S_i 's will not be ready at the same time
- We need to speed-up addition

CSE3201

Fall 2011

12

Carry Propagation


$$P_i = A_i \oplus B_i$$

$G_i = A_i B_i$ G is called the carry Generator
 $G_i = 1$ if A_i and $B_i = 1$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

Carry if either G_i or on of A, B and C

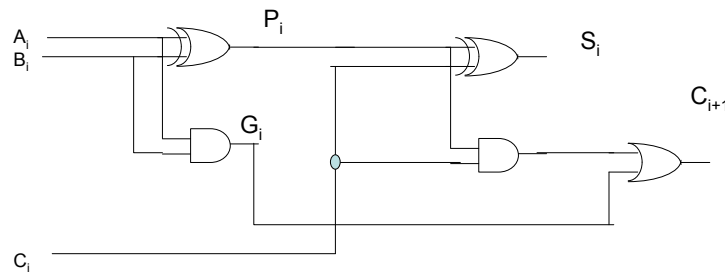

CSE3201

Fall 2011

13

Carry Lookahead

- G_i is called the carry Generator, and P_i is the carry propagate.
- We can calculate the carry at every stage by recursively substituting C_i

C_0 = input carry

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

Circuit in Figure 4-11

CSE3201

Fall 2011

14

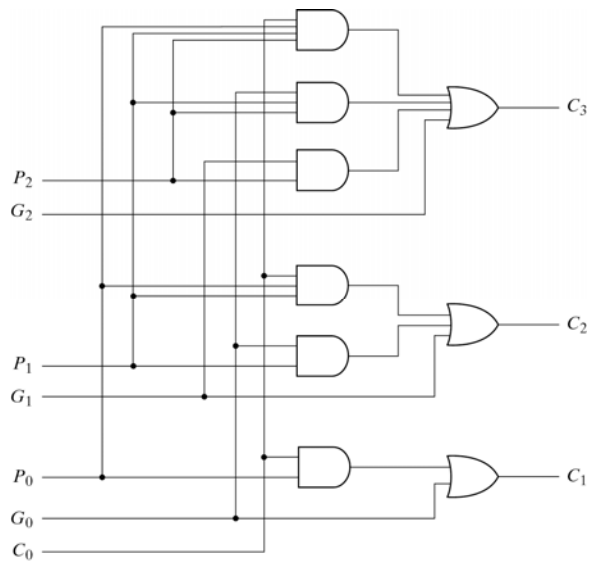


Fig. 4-11 Logic Diagram of Carry Lookahead Generator

CSE3201

Fall 2011

15

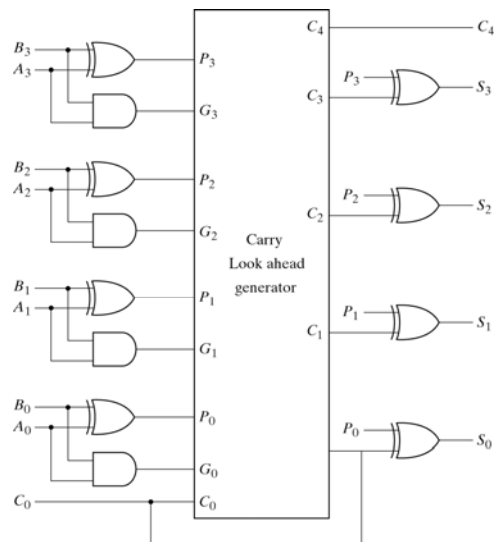



Fig. 4-12 4-Bit Adder with Carry Lookahead

CSE3201

Fall 2011

16

Adder/Subtractor

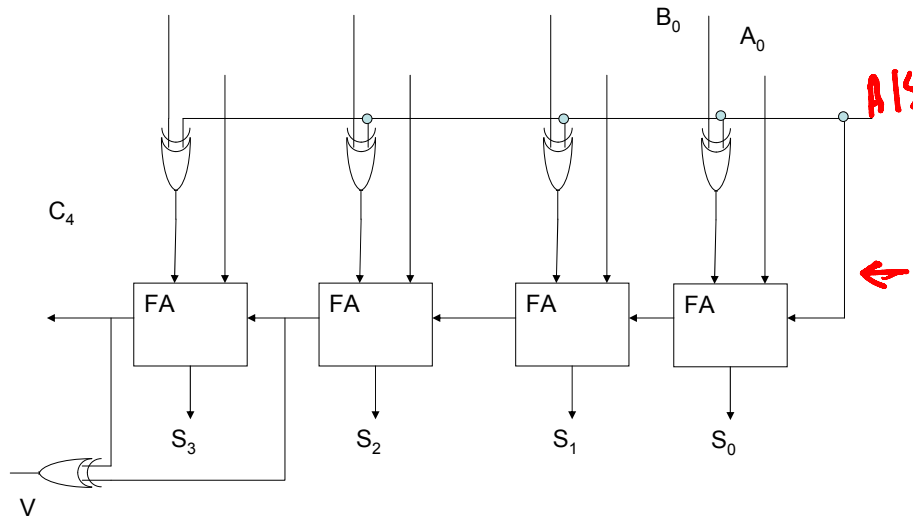

CSE3201

Fall 2011

17

Overflow

- When adding two n -bits number, the answer has a maximum of $n+1$ bits.
- If the numbers are represented in the computer by n bits, the $n+1^{\text{st}}$ bit is an overflow.
- Usually the overflow is detected and reported to the user.

CSE3201

Fall 2011

18

Overflow

+60 0 0111100
 +90 0 1011010

 1 0010110

-60 1 1000100
 +90 0 1011010

 1 0 0011110

-60 1 1000100
 -90 1 0100110

 1 0 1101010

An overflow is detected if the carry into the sign bit and the carry out of the sign bit is not the same

CSE3201

Fall 2011

19

Decimal Adder

Binary Sum

K	Z8	Z4	Z2	Z1
0	0	0	0	0
0	0	0	0	1
0	0	0	1	0
0	0	0	1	1
0	0	1	0	0
0	0	1	0	1
0	0	1	1	0
0	0	1	1	1
0	1	0	0	0
0	1	0	0	1
0	1	0	1	0
0	1	0	1	1
0	1	1	0	0
0	1	1	0	1
0	1	1	1	0
0	1	1	1	1
1	0	0	0	0
1	0	0	0	1
1	0	0	1	0
1	0	0	1	1

BCD Sum

K	Z8	Z4	Z2	Z1
0	0	0	0	0
0	0	0	0	1
0	0	0	1	0
0	0	0	1	1
0	0	1	0	0
0	0	1	0	1
0	0	1	1	0
0	0	1	1	1
0	1	0	0	0
0	1	0	0	1
1	0	0	0	0
1	0	0	0	1
1	0	0	1	0
1	0	0	1	1
1	0	1	0	0
1	0	1	0	1
1	0	1	1	0
1	0	1	1	1
1	1	0	0	0
1	1	0	0	1

Decimal

0
1
2
3
4
5
6
7
8
9
10
11
12
13
14
15
16
17
18
19

CSE3201

Fall 2011

20

Decimal Adder


- The output of the BCD could be anything between 0 and 19 (9+9+carry).
- From the truth table, it is clear that there is a carry (BCD carry) if any one of the following occurs
 1. $K = 1$ 1 (if the number is greater than 16).
 2. $Z_8=1$ and $Z_4=1$
 3. If $Z_8=1$ and $Z_2=1$
- If there is a carry, we must add 6 to the binary number to get the BCD code.
- That leads to the following circuit

CSE3201

Fall 2011

21

Decimal Adder

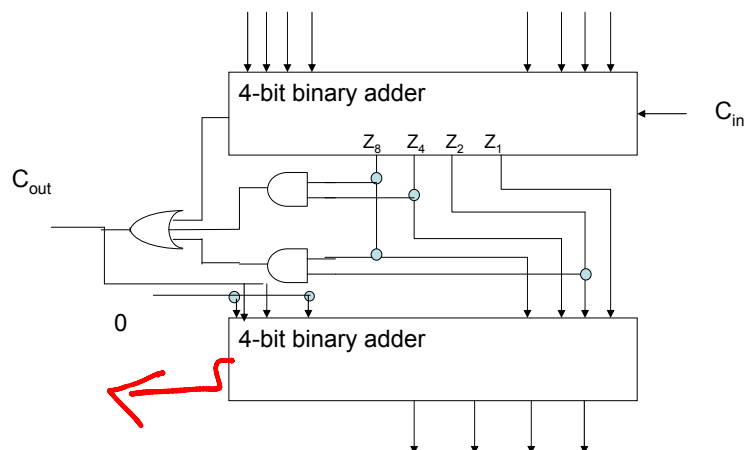


CSE3201

Fall 2011

22

Binary Multiplier


- First, consider 2 bit multiplier

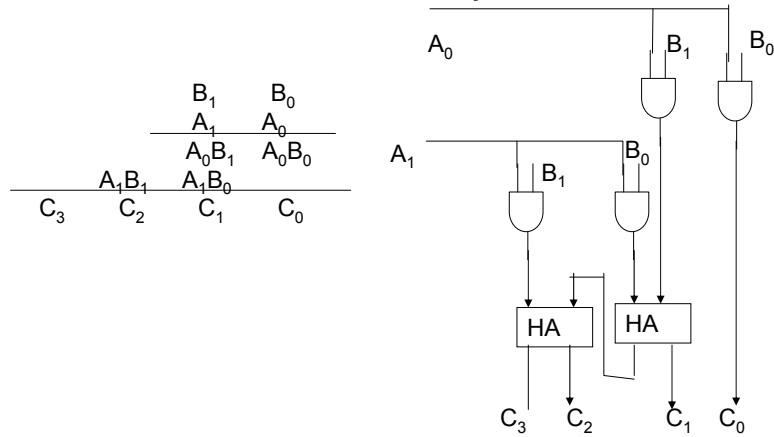

CSE3201

Fall 2011

23

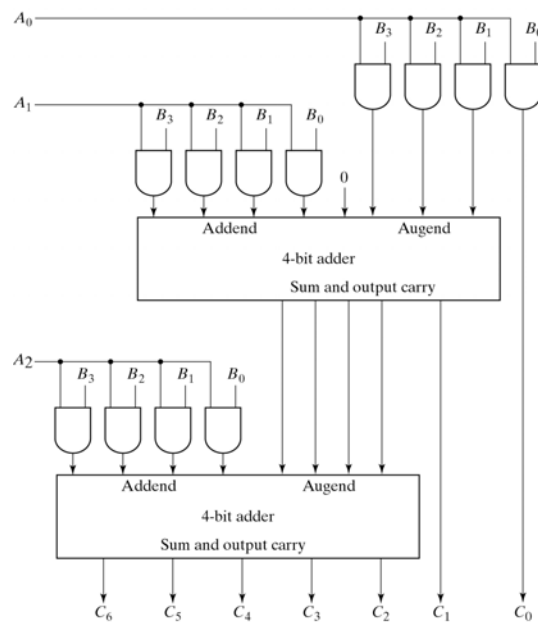

CSE3201

Fig. 4-16 4-Bit by 3-Bit Binary Multiplier

24

Magnitude Comparator

- Assume that we want to design a magnitude comparator for 2 4-bit numbers.
- Direct implementation of this requires a truth table with $2^8=256$ entries.
- It is easier to understand the algorithm by which we compare two numbers, that leads to a much less complicated design process.
- Assume the 2 numbers are represented as $A_3A_2A_1A_0$ and $B_3B_2B_1B_0$
- The algorithm works as follows

CSE3201

Fall 2011

25

Magnitude Comparator

- The two numbers are equal iff all the bits in the 2 numbers are equal. That leads to a design of 4EX-OR followed by inverter (actually ex-nor) and an or gate.
- For A to be greater than B, we must have $A_i > B_i$ and $A_j = B_j$ $j > i$.
- So, we start at digit 3, compare A_3 and B_3 , either one is greater or they are equal we move to A_2 and B_2 and so on.
- If we define x_i to be the ex-nor of A_i and B_i i.e. x_i is 1 if $A_i = B_i$

CSE3201

Fall 2011

26

Magnitude Comparator

- In this case,
- $(A=B)=x_3x_2x_1x_0$
- $(A>B)=A_3B'_3+x_3A_2B'_2 + x_3x_2A_1B'_1+x_3x_2x_1A_0B'_0$
- $(A<B)$ replace the prime from B to A.
- Circuit is shown in Figure 4-17

CSE3201

Fall 2011

27

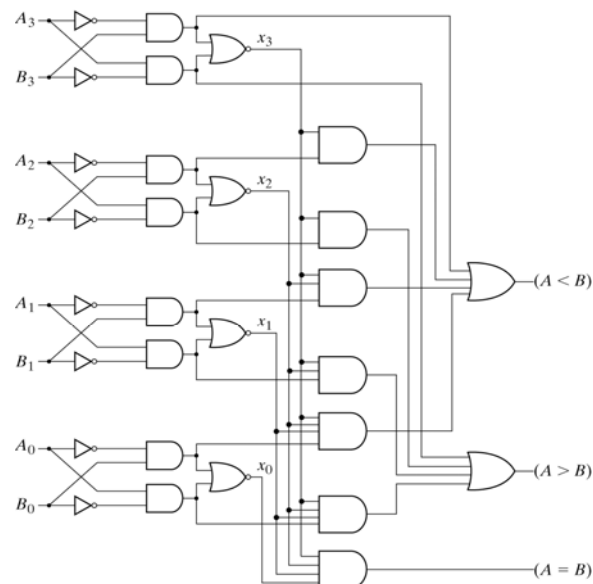


Fig. 4-17 4-Bit Magnitude Comparator
Fall 2011

CSE3201

28

Decoders

- A *decoder* is a combinational circuit that converts binary information from n inputs to a maximum of 2^n outputs.
- A decoder is called n -to- m decoder, where $m \leq 2^n$
- Consider 3-8 decoder, truth table with 3 inputs x, y, z and 8 outputs $D_7 \dots D_0$ the circuit is shown in Figure 4-18

CSE3201



Fall 2011

29

Decoders

X	Y	F ₀	F ₁	F ₂	F ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- From truth table, circuit for 2x4 decoder is:
- Note: Each output is a 2-variable minterm ($X'Y'$, $X'Y$, XY' or XY)

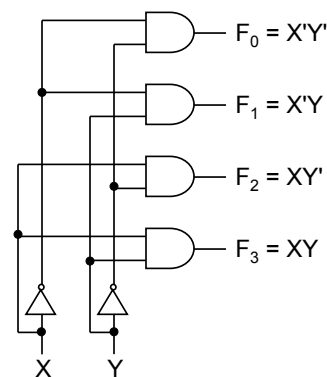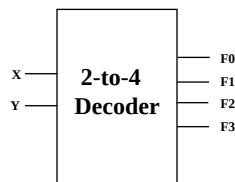



CSE3201

Fall 2011

30

Decoders

x	y	z	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

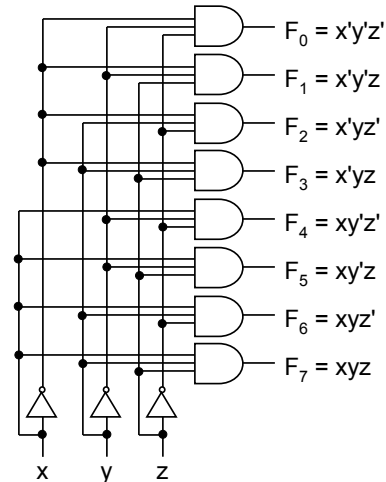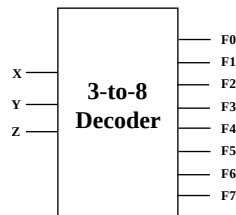

CSE3201

Fall 2011

31

Decoders

- Some decoders are implemented using NAND gates, in this case it will be more economical to produce the output in their complemented form.
- 2-4 decoder
- Circuit 4-19
- When E is 1, non
Of the outputs 1 0
- Decoder may be
Activated With E=0 or 1

E	A	B	D ₀	D ₁	D ₂	D ₃
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

CSE3201

Fall 2011

32

Decoders

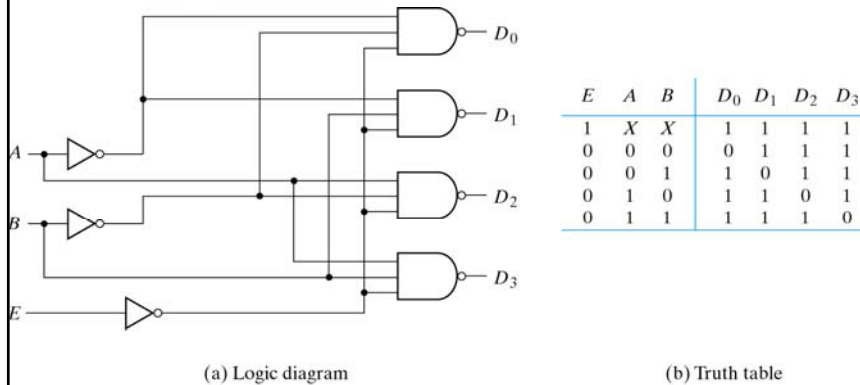


Fig. 4-19 2-to-4-Line Decoder with Enable Input

CSE3201

Fall 2011

33

Decoders

- A *decoder* with an *Enable* input can function as a *demultiplexer*
- A demultiplexer is a circuits that receives data from a single line, and direct it to a possible of 2^n lines (example sharing a communication line).
- The decoder in the previous slide can function as a demultiplexer if we consider E to be the data and A, and B to be the input selection.
- Verify this by assuming selection 10 and determine the output (always equal to E).


CSE3201

Fall 2011

34

Decoders

- Decoders with enable can be connected together to form a larger decoder

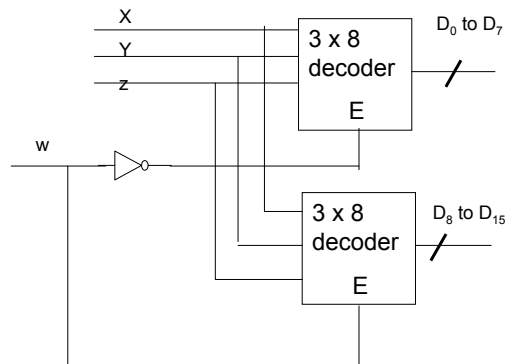

CSE3201

Fall 2011

35

Decoders

- Any n -variable logic function can be implemented using a single n -to- 2^n decoder to generate the minterms
 - OR gate forms the sum.
 - The output lines of the decoder corresponding to the minterms of the function are used as inputs to the or gate.
- Any combinational circuit with n inputs and m outputs can be implemented with an n -to- 2^n decoder with m OR gates.
- Suitable when a circuit has many outputs, and each output function is expressed with few minterms.


CSE3201

Fall 2011

36

Decoders

- Decoders can be used to implement logic functions.
- Consider the function $S(x,y,z) = \Sigma(0,1,3)$ and $C(x,y,z) = \Sigma(4,2)$
- Verify this by stating what will be the output if the input is any of the different combination in the truth table

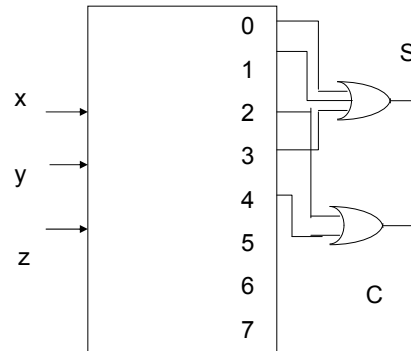


CSE3201


Fall 2011

37

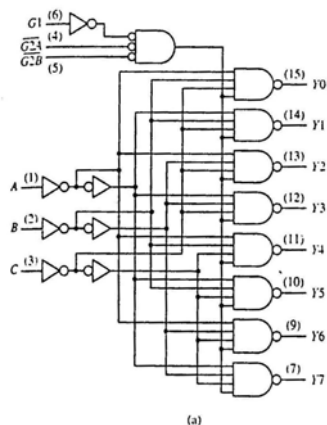Standard MSI Binary Decoders Example 74138 (3-to-8)



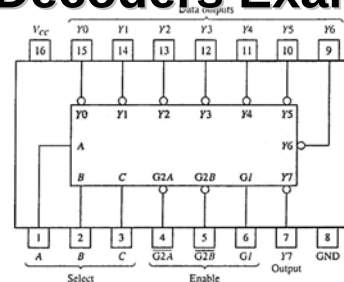(a) Logic circuit.
(b) Package pin configuration.
(c) Function table.



Inputs					Outputs							
Enable		Select			Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
G1	G2*	C	B	A								
H	L	L	L	L	L	H	H	H	H	H	H	H
H	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	H	L	H	H	L	H	H	H	H	H
H	L	L	H	H	H	H	H	L	H	H	H	H
H	L	H	L	L	H	H	H	H	L	H	H	H
H	L	H	L	H	H	H	H	H	H	L	H	H
H	L	H	H	L	H	H	H	H	H	H	L	H
H	L	H	H	H	H	H	H	H	H	H	H	L
L	x	x	x	x	L	x	x	x	x	x	x	x
L	x	x	x	x	L	x	x	x	x	x	x	x

$$G2^* = G2A + G2B$$

CSE3201

Fall 2011

38

Encoders

- Encoders perform the reverse operation of a decoder.
- An encoder has up to 2^n input lines, and n output lines.
- The encoder generates the binary code corresponding to the active input line.
- Truth table with 8 variables and three outputs, only need 1 in every row
- $x = D_1 + D_3 + D_5 + D_7$; $y = D_2 + D_3 + D_6 + D_7$;
 $z = D_4 + D_5 + D_6 + D_7$


CSE3201

Fall 2011

39

Encoders

Inputs								Outputs		
I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7	y_2	y_1	y_0
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

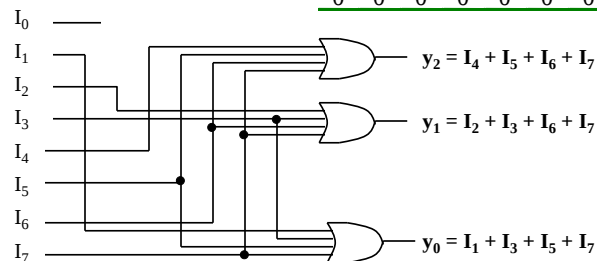

CSE3201

Fall 2011

40

Priority Encoders

- Priority encoders are encoders with a certain priority scheme.
- If more than one input is active, the one with the higher priority is encoded.
- The following figure shows the truth table for a priority encoder.
- Note that there is a valid bit. The valid bit indicates if the output is valid or not, if none of the input is active, the V bit is 0, means nothing is active

CSE3201

Fall 2011

41

Priority Encoders

- What if more than one input line has a value of 1?
- Ignore “lower priority” inputs.
- **Idle** indicates that no input is a 1.
- Note that **polarity of Idle is opposite from Table 4-8 in Mano**

Inputs								Outputs			Idle
I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇	y ₂	y ₁	y ₀	
0	0	0	0	0	0	0	0	x	x	x	1
1	0	0	0	0	0	0	0	0	0	0	0
X	1	0	0	0	0	0	0	0	0	1	0
X	X	1	0	0	0	0	0	0	1	0	0
X	X	X	1	0	0	0	0	0	1	1	0
X	X	X	X	1	0	0	0	1	0	0	0
X	X	X	X	X	1	0	0	1	0	1	0
X	X	X	X	X	X	1	0	1	1	0	0
X	X	X	X	X	X	X	1	1	1	1	0

CSE3201

Fall 2011

42

Priority encoders

- Assign priorities to the inputs
- When more than one input are asserted, the output generates the code of the input with the highest priority
- Priority Encoder :

$H7 = I7$ (Highest Priority)

$H6 = I6 \cdot I7'$

$H5 = I5 \cdot I6' \cdot I7'$

$H4 = I4 \cdot I5' \cdot I6' \cdot I7'$

$H3 = I3 \cdot I4' \cdot I5' \cdot I6' \cdot I7'$

$H2 = I2 \cdot I3' \cdot I4' \cdot I5' \cdot I6' \cdot I7'$

$H1 = I1 \cdot I2' \cdot I3' \cdot I4' \cdot I5' \cdot I6' \cdot I7'$

$H0 = I0 \cdot I1' \cdot I2' \cdot I3' \cdot I4' \cdot I5' \cdot I6' \cdot I7'$


$IDLE = I0' \cdot I1' \cdot I2' \cdot I3' \cdot I4' \cdot I5' \cdot I6' \cdot I7'$

- Encoder

$Y0 = I1 + I3 + I5 + I7$

$Y1 = I2 + I3 + I6 + I7$

$Y2 = I4 + I5 + I6 + I7$

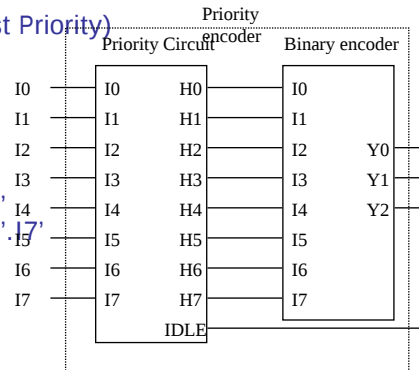

CSE3201

Fall 2011

43

Priority Encoders

Inputs Outputs

$D_0 \ D_1 \ D_2 \ D_3$ $x \ y \ z$

0 0 0 0 X X 0

1 0 0 0 0 0 1

X 1 0 0 0 1 1


X X 1 0 1 0 1

X X X 1 1 0 1

$X = D_2 + D_3$

$Y = D_3 + D_1 D_2'$

$V = D_0 + D_1 + D_2 + D_3$

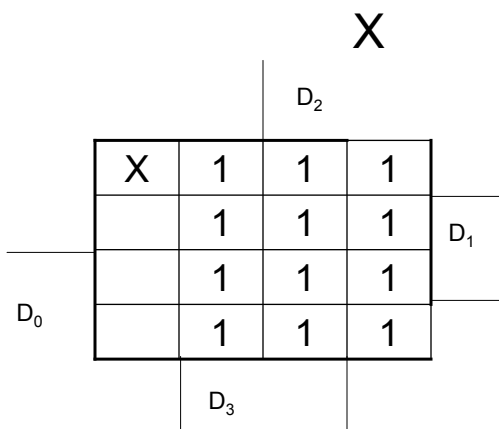


CSE3201

Fall 2011

44

Priority Encoders

- Encoder identifies the requester and encodes the value
- Controller accepts digital inputs.

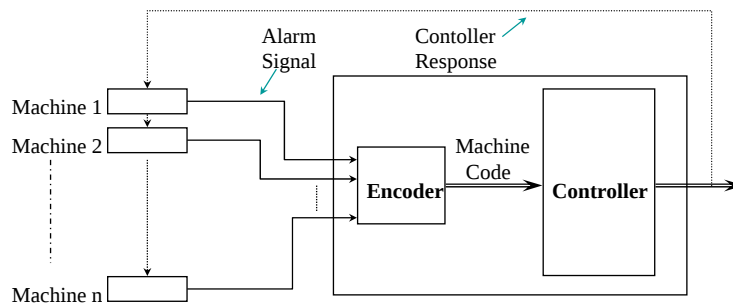

CSE3201

Fall 2011

45

Summary

- Decoder allows for generation of a single binary output from an input binary code
 - For an n -input binary decoder there are 2^n outputs
- Decoders are widely used in storage devices (e.g. memories)
 - We will discuss these in a few weeks
- Encoders allow for data compression
- Priority encoders rank inputs and encode the highest priority input

CSE3201

Fall 2011

46

Multiplexers

- A multiplexer is a combinational circuit that accepts binary information from one of many input lines and directs it to the output line.
- Which input to accept information from is selected by the selection lines.
- Usually there are n selection lines and 2^n input lines.
- A multiplexer can be combined with a common selection to select multiple bit selection, and Enable to control the operation. Figure 4-26 shows a quadruple 2-1 line multiplexer.

CSE3201

Fall 2011

47

Multiplexers


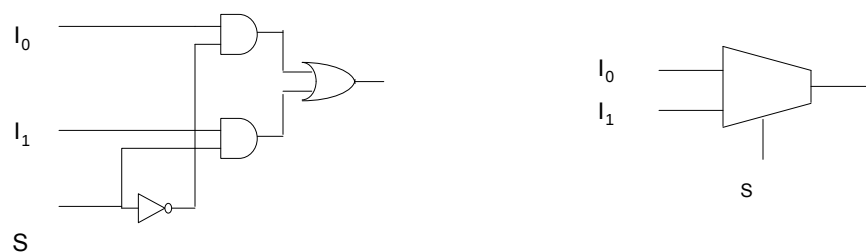


Figure 4-25

CSE3201

Fall 2011

48

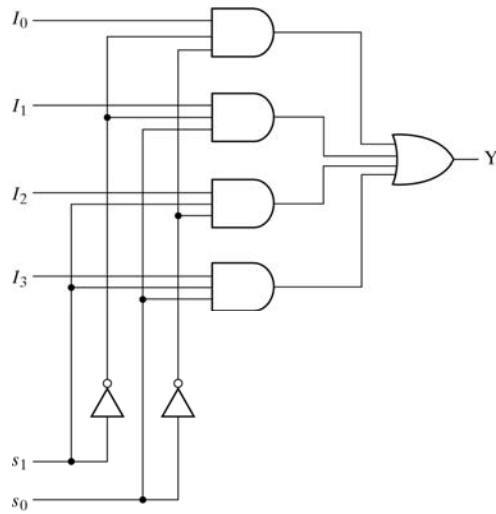

s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table


(a) Logic diagram

Fig. 4-25 4-to-1-Line Multiplexer

CSE3201

Fall 2011

49

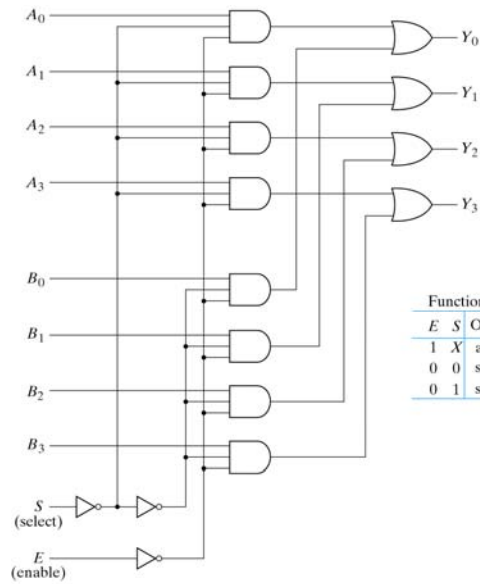

Function table		
E	S	Output Y
1	X	all 0's
0	0	select A
0	1	select B

Fig. 4-26 Quadrduple 2-to-1-Line Multiplexer

CSE3201

Fall 2011

50

Function Implementation

- We can consider the multiplexer to be a decoder that include the OR gates within.
- The OR minterms are generated by the function associated with the selection inputs.
- The rule to implement a function is as follows:

CSE3201

Fall 2011

51

Function Implementation

- Assume that we have n variables
- Choose $n-1$ of them to be the selection lines of a 2^{n-1} -to-1 multiplexer.
- The selection lines chooses one of 2^{n-1} inputs.
- These inputs corresponds to the the truth table (2^n) entries taken 2 entries at a time.
- Assume the n^{th} variable is Z .
- These 2^{n-1} entries each is Z , Z' , 0, or 1
- According to the entry number, the corresponding input is one of these 4 values. 4-27 and 4-28


CSE3201

Fall 2011

52

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(a) Truth table

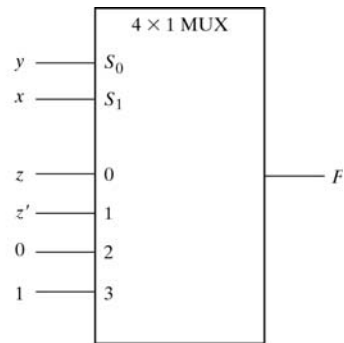

(b) Multiplexer implementation

Fig. 4-27 Implementing a Boolean Function with a Multiplexer

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


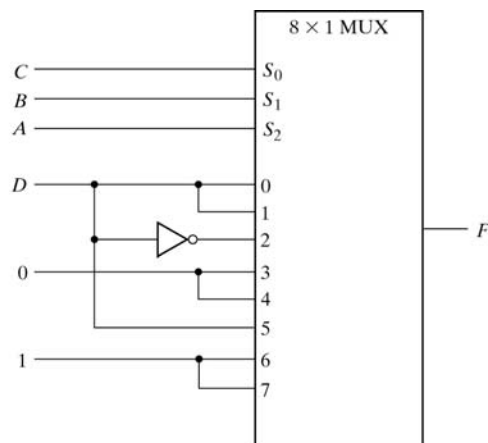


Fig. 4-28 Implementing a 4-Input Function with a Multiplexer

Three States gates

- The figure shows a three state buffer
$$Y = \begin{cases} Y = A & \text{if } C = 1 \\ Y = \text{High Z} & \text{if } C = 0 \end{cases}$$

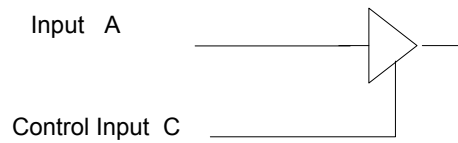


CSE3201

Fall 2011

55

Multiplexers with three-state gates

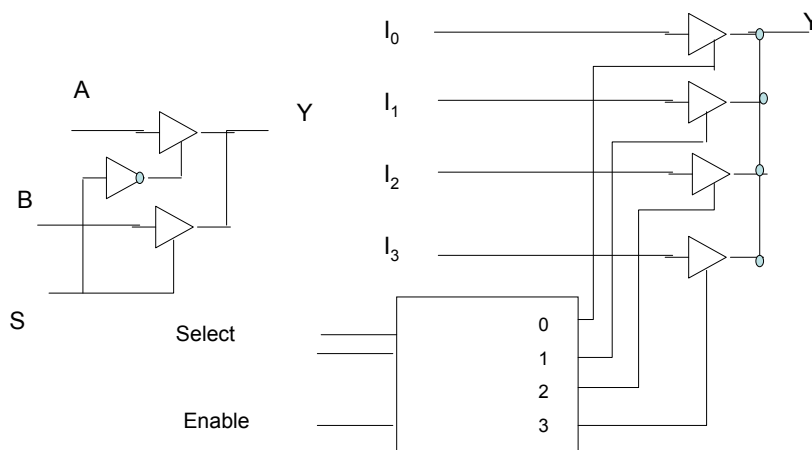

CSE3201

Fall 2011

56

HDL for Combinational Circuits

- A module in Verilog can be described in any one of the following modeling techniques
 - Gate-level modeling using instantiation of primitive gates and user-defined modules.
 - Dataflow modeling using continuous assignment statements with **assign**
 - Behavioral modeling using procedural assignment statements with **always**

CSE3201

Fall 2011

57

Verilog (gate-level)

- In gate level we have the following primitive gates (**and, nand, or, nor xor, xnor, not, buf**)
- The system assigns four-valued logic to every gate (0,1,z,x).
- The truth tables for the 4 most used gates is shown in the next slide

CSE3201

Fall 2011

58

Verilog

```

and 0 1 x z
0    0 0 0 0
1    0 1 x x
x    0 x x x
z    0 x x x

```

```

xor 0 1 x z
0    0 1 0 0
1    1 0 x x
x    x x x x
z    x x x x

```

```

Or 0 1 x z
0    0 1 x x
1    1 1 1 1
x    x 1 x x
z    x 1 x x

```

```

not Input  output
      0       1
      1       0
      x       x
      z       x

```

CSE3201

Fall 2011

59

Verilog 2-4 line decoder

```

//gate-level description of a 2-4 line decoder
module decoder_g1(A,B,E,D);
  input      A,B,E;
  output     [0:3]D;
  wire Anot, Bnot, Enot;
  not
    n1(Anot,A),
    n2(Bnot,B),
    n3(Enot,E);
  nand
    n1(D[0],Anot,Bnot,Enot),
    n2(D[1],Anot,B,Enot),
    n3(D[2],A,Bnot,Enot),
    n4(D[3],A,B,Enot);
endmodule


```

CSE3201

Fall 2011

60

Three-state Gates

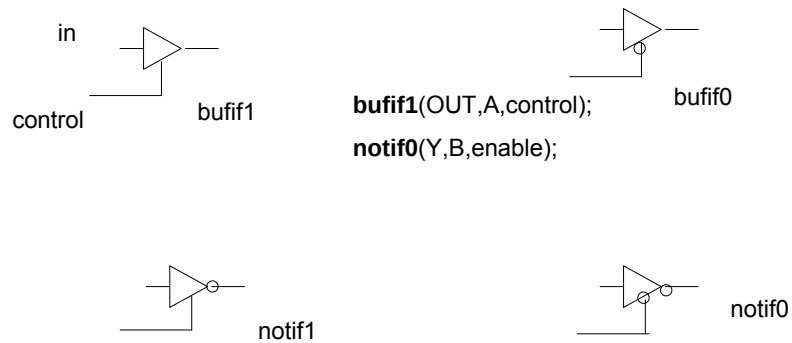


```
bufif1(OUT,A,control);
notif0(Y,B,enable);
```

CSE3201

Fall 2011

61

Three State Gates

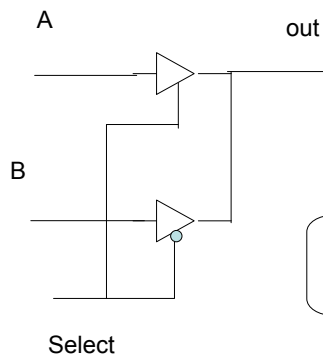

```
module muxtri(A,B,select,OUT);
  input A,B,select
  output OUT;
  tri OUT;
  bufif1(OUT,A,select);
  bufif0(OUT,B,select);
endmodule
```

must be
tri

CSE3201

Fall 2011

62

Dataflow Modeling

```
//Dataflow modeling of a 2-4 line decoder
module decoder_df (A,B,E,D);
  input A,B,E;
  output [0:3] D;
  assign      D[0]=~(~A & ~B & ~E),
              D[1]=~(~A &  B & ~E),
              D[2]=~( A & ~B & ~E),
              D[3]=~( A &  B & ~E);
endmodule
```

Dataflow Modeling

```
//Dataflow modeling of a 4-bit adder
module binary_adder (A,B,C_in,SUM,C_OUT);
  input [3:0]A,B;
  input C_in;
  output [3:0] SUM;
  output C_out;
  assign {C_out,SUM} = A+B;
endmodule
```

Dataflow Modeling

```
//Dataflow Modeling of a 4-bit  
comparator  
module magcomp (A,B,ALSB,AGTB,AEQB);  
  input [3:0] A,B;  
  output ALTB, AGTB,AEQB;  
  assign ALTB = (A < B),  
          AGTB = (A>B),  
          AEQB = (A==B);  
endmodule
```

CSE3201

Fall 2011

65

Dataflow Modeling

```
//Dataflow model for a 2-to-1 mux  
module mux2x1_df(A,B,select,OUT);  
  input A,B,select;  
  output OUT;  
  assign OUT= select? A : B;  
endmodule
```

CSE3201

Fall 2011

66

behavioral description

```
//Behavioral description of a 2-1 line MUX
module mux2_1 (A,B,select,OUT);
  input A,B,select;
  output OUT;
  reg OUT;
  always @ (select or A or B)
    if (select == 1) OUT = A;
    else OUT=b;
endmodule
```

CSE3201

Fall 2011

67

Simulation (Test Bench)

- A test bench is a program for applying simulation to an HDL design.
- initial statements are executed at time 0
- always statements are executed always
- test module has no input or outputs
- The signals that are applied to the design module are declared as **reg**.
- The output of the design modules are declared as **wire**.

CSE3201

Fall 2011

68

4-to-1 MUX

- Description of a 4-to-1 MUX using conditional
- operators:

```
module mux4to1 (w0, w1, w2, w3, S, f);  
    input w0, w1, w2, w3;  
    input [1:0] S;  
    output f;  
    assign f = S[1] ? (S[0] ? w3 : w2) : (S[0] ? w1 : w0);  
endmodule
```

```
module mux4to1 (W, S, f);  
    input [0:3] W;  
    input [1:0] S;  
    output f;  
    reg f;  
    always @(*)  
    if (S == 0)  
        f = W[0];  
    else if (S == 1)  
        f = W[1];  
    else if (S == 2)  
        f = W[2];  
    else if (S == 3)  
        f = W[3];  
endmodule
```

□ Description of a 4-to-1 MUX using a case statement:

```
module mux4to1 (W, S, f);  
input [0:3] W;  
input [1:0] S;  
output f;  
reg f;  
always @(*)  
    case (S)  
        0: f = W[0];  
        1: f = W[1];  
        2: f = W[2];  
        3: f = W[3];  
    endcase  
endmodule
```

CSE3201

Fall 2011

71

□ Verilog description of a priority encoder:

```
module priority (W, Y, z);  
input [3:0] W;  
output [1:0] Y;  
output z;  
reg [1:0] Y;  
reg z;  
always @(*)  
    begin  
        z = 1;  
        case (W)  
            4'b1xxx: Y = 3;  
            4'b01xx: Y = 2;  
            4'b001x: Y = 1;  
            4'b0001: Y = 0;  
            default: begin  
                z = 0;  
                Y = 2'bxx;  
            end  
        endcase  
    end  
endmodule
```

CSE3201

Fall 2011

72

□ Verilog description of a 16-to-1 MUX constructed as a tree of 4-to-1 decoders:

```
module mux16to1 (W, S, f, M);  
    input [0:15] W;  
    input [3:0] S;  
    output f;  
    output [3:0] M;  
    wire [0:3] M;  
    mux4to1 Mux1 (W[0:3], S[1:0], M[0]);  
    mux4to1 Mux2 (W[4:7], S[1:0], M[1]);  
    mux4to1 Mux3 (W[8:11], S[1:0], M[2]);  
    mux4to1 Mux4 (W[12:15], S[1:0], M[3]);  
    mux4to1 Mux5 (M[0:3], S[3:2], f);  
endmodule
```