

Chapter 3

Pipelining and parallel Processing

CSE4210 Winter 2012

Mokhtar Aboelaze


YORK UNIVERSITY

CSE4210

Pipelining -- Introduction


- Pipelining can be used to reduce the the critical path.
- That can lead to either increasing the clock speed, or decreasing the power consumption
- Multiprocessing can be also used to increase speed or reduce power.

Pipelining

 

The critical path here is two additions and one multiplication
 
$$T_s = 2T_{add} + T_{mul} \quad , \quad f_s = \frac{1}{(2T_{add} + T_{mul})}$$



Pipelining

Parallel processing


Pipelining

- Advantages
 - Could be used to reduce power and/or to increase clock rate (speed)
- Disadvantages
 - Increases number of delay elements (latches or flip-flops)
 - Increases latency


Pipelining

- **Cutset**: is a set of edges of a graph if removed, the graph becomes partitioned
- **Feed forward cutset**: a cutset where the data moves in the forward direction on all the edges in the cutset
- We can place latches on a **feed-forward cutset** without affecting the functionality of the graph.

Pipelining

 


Example

 

Data Broadcast Structures

- Reversing the direction of all the edges in a given SFG, and interchanging the input and output preserves the functionality of the system.

Data Broadcast

 


Fine-Grain Pipelining


Multiplication time = 10

Addition time = 2

Critical path = ?

 

Fine grain Pipelining

 



Parallel Processing

$$y(n) = ax(n) + bx(n-1) + cx(n-2)$$


$$y(3k) = ax(3k) + bx(3k-1) + cx(3k-2)$$

$$y(3k+1) = ax(3k+1) + bx(3k) + cx(3k-1)$$

  
$$y(3k+2) = ax(3k+2) + bx(3k+1) + cx(3k)$$



Complete Parallel System

 


S/P and P/S Converter

 

Parallel Processing

 - Why use parallel processing? It increases the hardware.
- There is a limit for the use of pipelining, you may not be able to pipeline a functional unit beyond a certain limit
- Also, I/O usually imposes a bound on the cycle time (communication bound)



Low Power

$$P = C_{total} V_o^2 f$$

$$T_{pd} = \frac{C_{charge} V_o}{k(V_o - V_t)^2} \quad \text{Simple approximation for CMOS}$$

C_{total} is the total capacitance of the circuit, V_o is the supply voltage. C_{charge} is the capacitance to be charged/discharged in a single clock cycle.


Pipelining and parallel processing could be used to minimize power or execution time.

Low Power

- What happens in case of M –pipelining?
- Critical path is reduced by M , so is C_{charge}
- If we keep the same f , then we have more time to charge C_{charge} , which means we can reduce the supply voltage

$$T_{seq} = \frac{C_{charge} V_o}{k(V_o - V_t)^2} = T_{pip} = \frac{\frac{C_{charge}}{M} \beta V_o}{k(\beta V_o - V_t)^2}, P = ?$$

Low Power —Example

 

Example


Parallel processing

- What happen for L parallel System?
- Total capacitance increased by L
- Same performance, increase T by L
- More time to charge C_{charge} , can decrease V

$$LT_{seq} = L \frac{C_{charge} V_o}{k(V_o - V_t)^2} = T_{par} = \frac{C_{charge} \beta V_o}{k(\beta V_o - V_t)^2}, P = ?$$

Parallel Processing Example

- Consider a 4-tap FIR filter shown in Fig. 3.18(a) and its 2-parallel version in 3.18(b). The parallel filter has exactly 2 copies of the original filter. The dashed line donates the critical path.
- Assume Also that $T_M=8$, $T_A=1$, $V_t=0.45V$, $V_o=3.3V$, $C_M=8C_A$
 - What is the supply voltage of the 2-parallel filter?
 - What is the power consumption of the 2-parallel filter as a percentage of the original filter?

 

YORK UNIVERSITY CSE4210

Example

Different Architecture

 


Fig. 3.18 (a) A 4-tap FIR filter. (b) A 2-parallel filter. (c) An area-efficient 2-parallel filter.