

Computer Science and Engineering 2021.03

Sample Final Test

Answer all questions in the space provided

Student Last Name: _____

Student Given Name: _____

Student Id. No: _____

Question	Value	Score
1	30	
2	20	
3	50	

Question 1. [30 points, 10 such questions]

1. [3 points] In the standard carry-lookahead we make use of two signals g and p . What is their proper name?

2. [3 points] What is the disadvantage of one-bit branch prediction.

3. [3 points] What are the three types of hazards in pipelines.

4. [3 points] What is the simplest hardware technique to reduce the stalls due to hazards like

```
slli    x5, x5, 3
add     x5, x5, x10
```

5. [3 points] What is the basic principle that guides the design of memory hierarchies

6. [3 points] Inside what Verilog construct can we have a repeat statement.

7. [3 points]

8. [3 points]

9. [3 points]

10. [3 points]

Question 2.

[20 points]

1. [7 points]

2. [7 points] Write the truth table for the following logic function

$$F = A + BC + B'C'$$

Question 3.

[50 points]

1. [20 points] Assume you are given a module called `incr` that implements a combinational circuit that has a four bit input and a four bit output. The output is the input plus one. Write a simple Verilog module that has an one bit input `C`, another one bit input `pulse` and a four bit output `Z`. The output is normally zero when the input `C` is zero, but when the input `C` becomes one, then at the next sixteen pulses (`pulse`) the circuit counts from zero to fifteen and back to zero (i.e. 0, 1, 2, ..., 14, 15, 0, 1...)

2. [7 points] Write three versions of a module that implements a half adder using

- (1) the `always` construct of Verilog
- (2) the `assign` construct
- (3) the primitive gates AND, OR, NOT.