CSE4210 Architecture and Hardware for DSP


Chapter 6
Folding

Folding

- The folding transformation is used to systematically determine the control circuits in DSP architecture where multiple algorithm operations are time-multiplexed to a single functional unit.
- The hardware is reduced by a factor of N, the time is increased by the same factor.
- May lead to a large number of registers, thus registers minimization techniques are studied.

York University

CSE

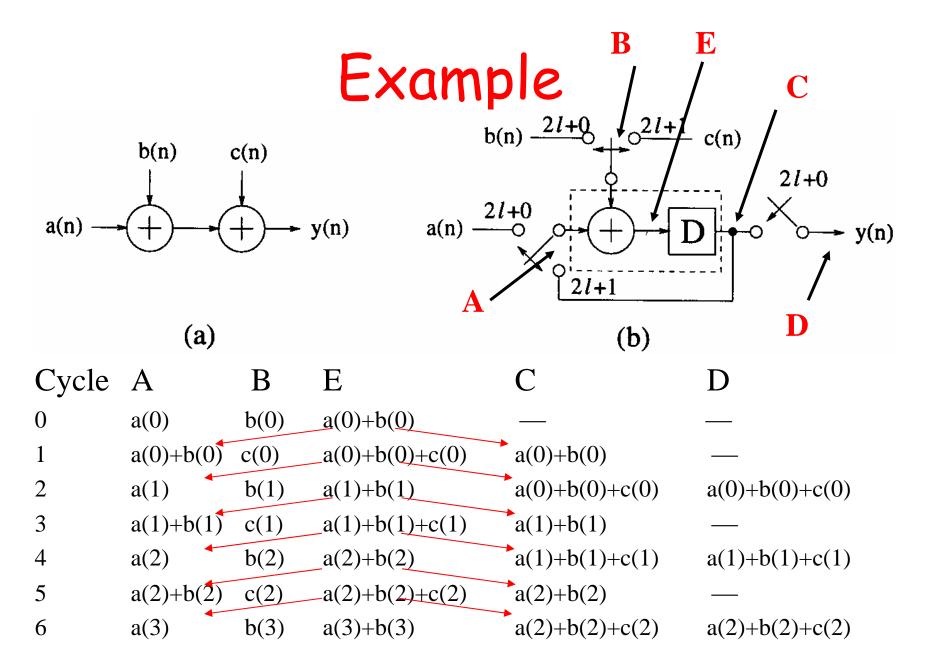


- The objective is to provide a systematic technique for designing control circuits for hardware where several algorithm operations are mapped to the same piece of hardware via time-multiplexing of course.
- · We start with a DFG for the algorithm.
- · We need the following definitions

- U and V are two nodes in the original DFG.
- U and V are connected via an edge e with a delay w(e) $U \xrightarrow{w(e)} V$
- Folding factor is N
- Node (computation) U l^{th} iteration is performed at time Nl +u
- Node (computation) V_l^{th} iteration is performed at time $N_l + v$, u and v are the folding order of U and V < N-1 (time partition scheduled for).
- H_u and H_v are the hardware units U and V are performed at
- H_u and H_v are pipelined by P_u and P_v stages

- The results of the l^{th} iteration of node U is available at $Nl+u+P_u$
- Since there are w(e) delays between U and V, the result is needed in the $(l+w(e))^{th}$ iteration of V, which is executed at N(l+w(e))+v, we need to store it for

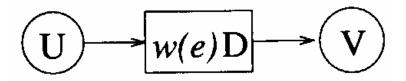
$$D_F(U \xrightarrow{e} V) = [N(l+w(e))+v]-[Nl+P_u+u]$$
$$= Nw(e)-P_u+v-u$$



Folding Set


- Is an ordered set of operations executed by the same functional unit.
- Each folding set contains N entries (some of which may be null operations)
- The Jth position within the folding set is executed in the time partition j
- For example the folding set $S_1 = \{A_1, \phi, A_2\}$ for N=3
- A_1 is performed during the 0^{th} time partition $S_1|0$, while A_2 is done in the 2^{nd} time partition $S_1|2$
- Folding set is obtained using a scheduling and allocation algorithm

Example

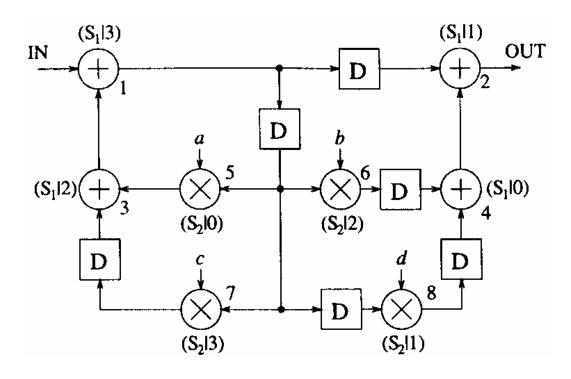

- $\square N=4$
- □ Folding sets are adder S_1 ={4,2,3,1} and a multiplier S_2 ={5,8,6,7}
- ☐Addition takes 1 and multiplication 2 time units
- □1-stage adder and 2-stage multiplier

Example

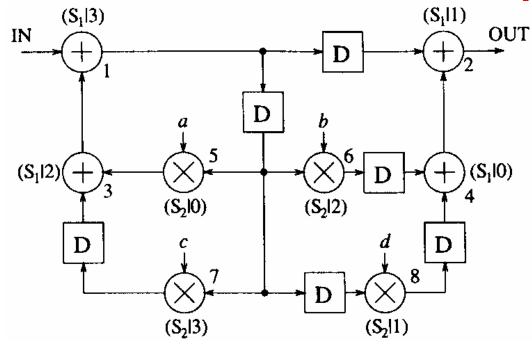

$$D_{F}(1 \to 2) = 4(1) - 1 + 1 - 3 = 1$$

$$D_{F}(1 \to 5) = 4(1) - 1 + 0 - 3 = 0$$

$$D_{F}(1 \to 6) = 4(1) - 1 + 2 - 3 = 2$$

$$D_{F}(1 \to 7) = 4(1) - 1 + 3 - 3 = 3$$

$$D_{F}(1 \to 8) = 4(2) - 1 + 1 - 3 = 5$$

$$D_{F}(3 \to 1) = 4(0) - 1 + 3 - 2 = 0$$

$$D_{F}(4 \to 2) = 4(0) - 1 + 1 - 0 = 0$$


$$D_{F}(5 \to 3) = 4(0) - 2 + 2 - 0 = 0$$

$$D_{F}(6 \to 4) = 4(1) - 2 + 0 - 2 = 0$$

$$D_{F}(7 \to 3) = 4(1) - 2 + 2 - 3 = 1$$
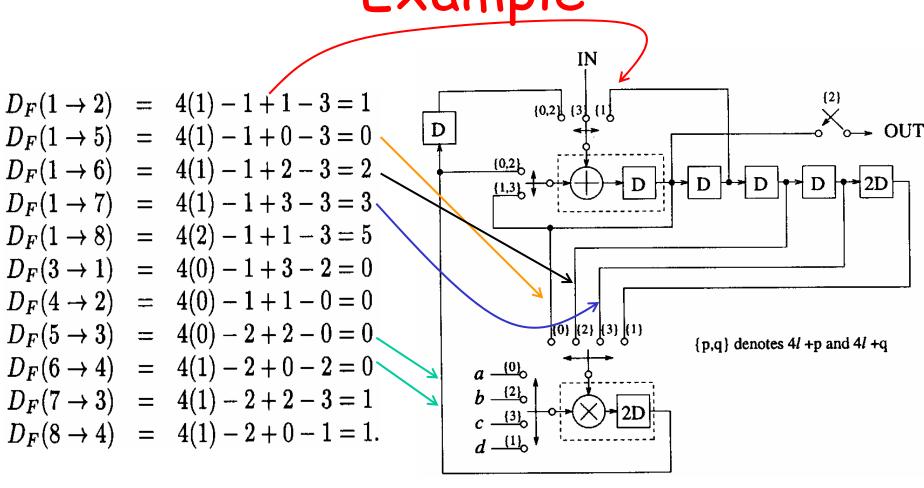
$$D_{F}(8 \to 4) = 4(1) - 2 + 0 - 1 = 1$$






- What if some of the D_F 's are negative
- · Of course we can not implement that
- A condition: $D_F \ge 0$
- · We can use retiming of the original graph to get a valid D_F 's
- · Recall, retiming equation

$$w_r(e) = w(e) + r(V) - r(U) \ge 0$$

$$\begin{split} D_F' & (U \stackrel{e}{\longrightarrow} V) \text{ is the delays in the folded retimed graph} \\ D_F & (U \stackrel{e}{\longrightarrow} V) = Nw(e) - P_u + v - u \\ D_F' & (U \stackrel{e}{\longrightarrow} V) = N\Big(w(e) + r(V) - r(U)\Big) - P_u + v - u \\ D_F' & (U \stackrel{e}{\longrightarrow} V) = Nw(e) - P_u + v - u + Nr(V) - Nr(U) \\ D_F' & (U \stackrel{e}{\longrightarrow} V) = D_F & (U \stackrel{e}{\longrightarrow} V) + Nr(V) - Nr(U) \ge 0 \\ r(U) - r(V) \le \frac{D_F & (U \stackrel{e}{\longrightarrow} V)}{N} \\ r(U) - r(V) \le \frac{D_F & (U \stackrel{e}{\longrightarrow} V)}{N} \\ \end{split}$$

- We can use the techniques in Chapter 4 to solve for retiming.
- Then we fold the graph → valid transformation


Exercise

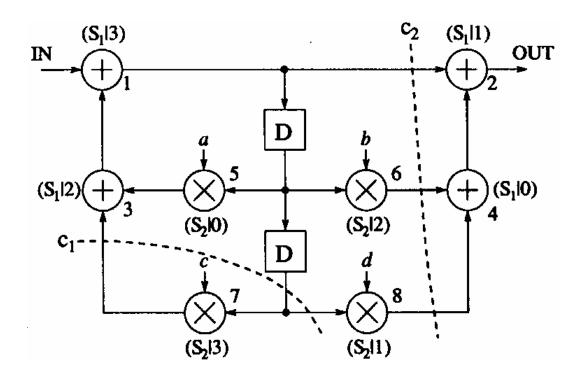

Exercise

| $\overline{\text{Edge}}$ | Folding Equation | Retiming for Folding Constraint |
|--------------------------|---------------------|---------------------------------|
| $1 \rightarrow 2$ | $D_F(1\to 2)=-3$ | $r(1)-r(2) \leq -1$ |
| $1 \rightarrow 5$ | $D_F(1 \to 5) = 0$ | $r(1) - r(5) \le 0$ |
| $1 \rightarrow 6$ | $D_F(1 \to 6) = 2$ | $r(1) - r(6) \le 0$ |
| $1 \rightarrow 7$ | $D_F(1 \to 7) = 7$ | $r(1)-r(7)\leq 1$ |
| $1 \rightarrow 8$ | $D_F(1 \to 8) = 5$ | $r(1)-r(8)\leq 1$ |
| $3 \rightarrow 1$ | $D_F(3\to 1)=0$ | $r(3) - r(1) \le 0$ |
| $4 \rightarrow 2$ | $D_F(4\to 2)=0$ | $r(4) - r(2) \le 0$ |
| $5 \rightarrow 3$ | $D_F(5\to 3)=0$ | $r(5) - r(3) \le 0$ |
| $6 \rightarrow 4$ | $D_F(6 \to 4) = -4$ | $r(6)-r(4)\leq -1$ |
| $7 \rightarrow 3$ | $D_F(7\to 3)=-3$ | $r(7) - r(3) \le -1$ |
| $8 \rightarrow 4$ | $D_F(8\to 4)=-3$ | $r(8)-r(4)\leq -1$ |

Exercise

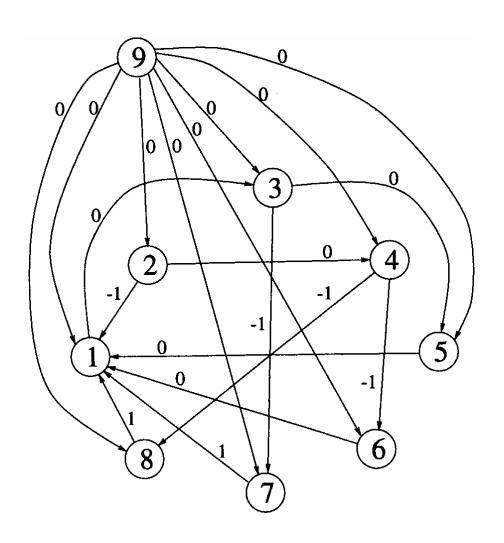

Registers Minimization Techniques

- The objective is to minimize the number of registers in the implementation of a DSP algorithm. Topics
 - >Life time analysis
 - Data allocation using forward-backward register allocation
 - > Register minimization in folded architecture
 - > Examples


Life Time Analysis


- A data sample (variable) is alive from the time it is produced, until the time it is consumed (dead).
- During that time, the variable is stored in a register.
- The maximum number of live variables at any time is the minimum number of registers required for the implementation.
- We use the convention that the variable is not alive during the cycle it is produced in, and alive during the cycle it is consumed in.

York University

CSE


| cycle | a | b | C | # live |
|-------|-------------|---|----------|------------|
| 0 - | | | | 0 |
| 1 - | | | | - 1 |
| 2 - | | + | | - 2 |
| 3 - | | 十 | | - 2 |
| 4 - | \multimap | + | 1 | - 2 |
| 5 - | | + | ╁ | - 2 |
| 6 - | | + | ╂ | - 2 |
| ž - | | O | <u>\</u> | - 2 |

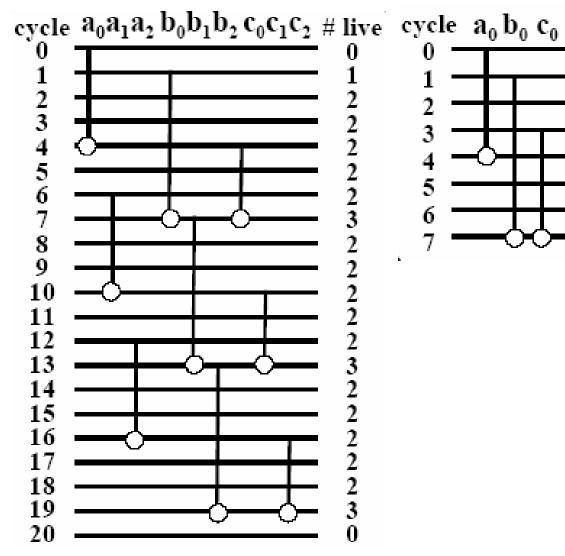

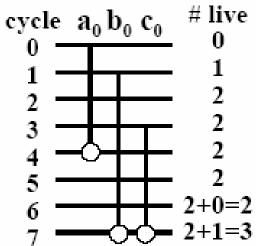

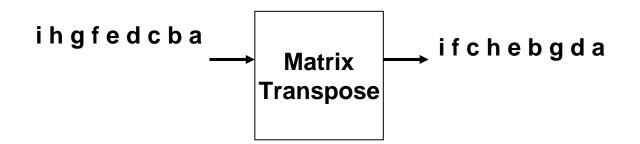Example


$$\begin{bmatrix} a & b & c \\ d & e & f \\ g & h & i \end{bmatrix} \qquad \text{Transpose} \qquad \begin{bmatrix} a & d & g \\ b & e & h \\ c & f & i \end{bmatrix}$$



Example

| Sample | T_{input} | T_{zout} | T_{diff} | Toutput | Life |
|--------|-------------|------------|------------|---------|--------------------|
| a | 0 | 0 | 0 | 4 | 0->4 |
| b | 1 | 3 | 2 | 7 | $1 \rightarrow 7$ |
| c | 2 | 6 | 4 | 10 | $2 \rightarrow 10$ |
| d | 3 | 1 | -2 | 5 | $3 \rightarrow 5$ |
| e | 4 | 4 | 0 | 8 | $4 \rightarrow 8$ |
| f | 5 | 7 | 2 | 11 | $5 \rightarrow 11$ |
| g | 6 | 2 | -4 | 6 | $6 \rightarrow 6$ |
| h | 7 | 5 | -2 | 9 | $7 \rightarrow 9$ |
| i | 8 | 8 | 0 | 12 | $8 \rightarrow 12$ |

Circular Life-Time Chart

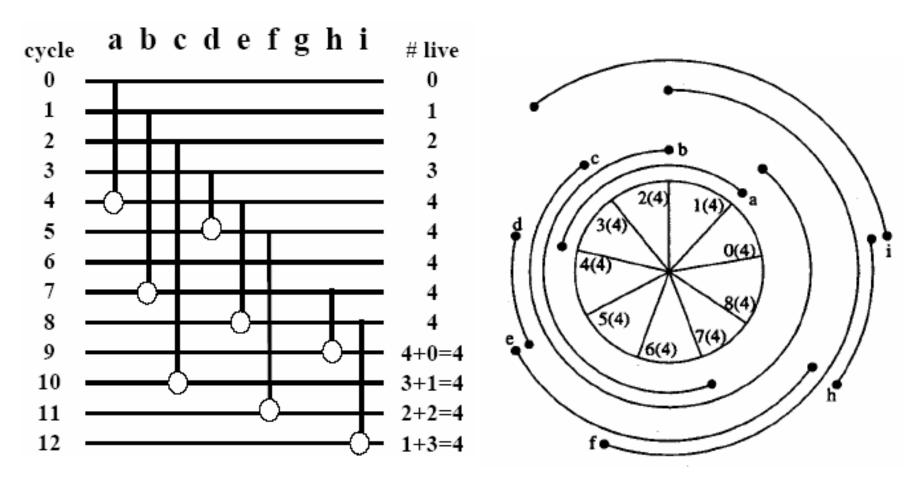

Data Allocation

- · Determine the min. number of rgisters
- Input each variable at the time its life starts. If more than one use multiple registers such that the longest lifetime is allocated to the initial register.
- · Each variable is allocated in a forward manner until it is dead or reaches the last register
- Allocation is periodic, all allocation to current iteration repeats itself after after N
- If reaches the last register and not dead allocate backward ((if more than one, choose one that has been allocated backward before), then forward again and so on.

| cycle | 2 | ı l |) (| e d | e 1 | f g | h | i | # live |
|-------|----|-----|-----|----------|-----|-----|----------|---|-----------|
| 0 | | | | | | | | _ | 0 |
| 1 | _ | | | | | | | _ | 1 |
| 2 | - | Н | Н | | | | | _ | 2 |
| 3 | - | Н | Н | | | | | _ | 3 |
| 4 | _(| ЪН | Н | - | _ | | | _ | 4 |
| 5 | _ | _ | Ш | | L | | | _ | 4 |
| 6 | _ | | Ш | | Н | | | _ | 4 |
| 7 | | لم_ | Ъ | | Ц | | - | _ | 4 |
| 8 | _ | | _ | | Ч | | Д, | _ | 4 |
| 9 | | | | | 1 | | 싀 | L | 4+0=4 |
| 10 | | | _, | <u> </u> | _ | | <u> </u> | | 3+1=4 |
| 11 | | | _ | | _/ | | | L | 2+2=4 |
| 12 | | | | | | | | Ļ | 1+3=4 |
| 12 | | | | | | | • | • | 1 1 J - T |

| Cycle | I/P | R1 | R2 | R3 | R4 | O/P |
|-------|-----|--------|-----|----|-----|-----|
| 0 | a < | | | | | |
| 1 | b | a . | | | | |
| 2 | c \ | p, | a | | | |
| 3 | d 、 | c | Ъ | à | | |
| 4 | e 、 | d | c | b | a | a |
| 5 | f | , e | d | Ĉ | b | d |
| 6 | g | f, | è | b | _ c | g |
| 7 | h 、 | c . | f, | e | b | b |
| 8 | i、 | ħ | c | f | e | e |
| 9 | | 1 , | ĥ | c | f | h |
| 10 | | | i , | f | c | c |
| 11 | | | | i | f | f |
| 12 | | | | | 1 | i |
| | | | | | | |
| ļ | | | I | I | I | 1 |